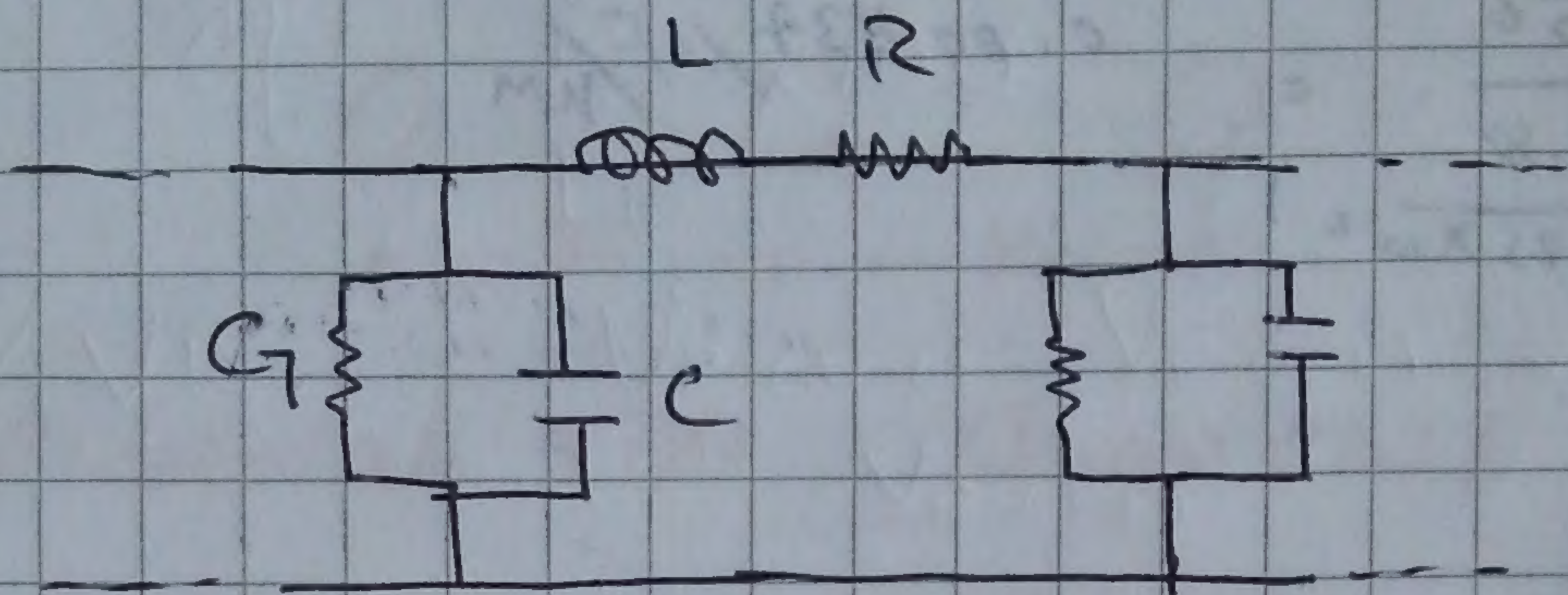




A.G


28-3-2017

lecture 9



[Conductance]

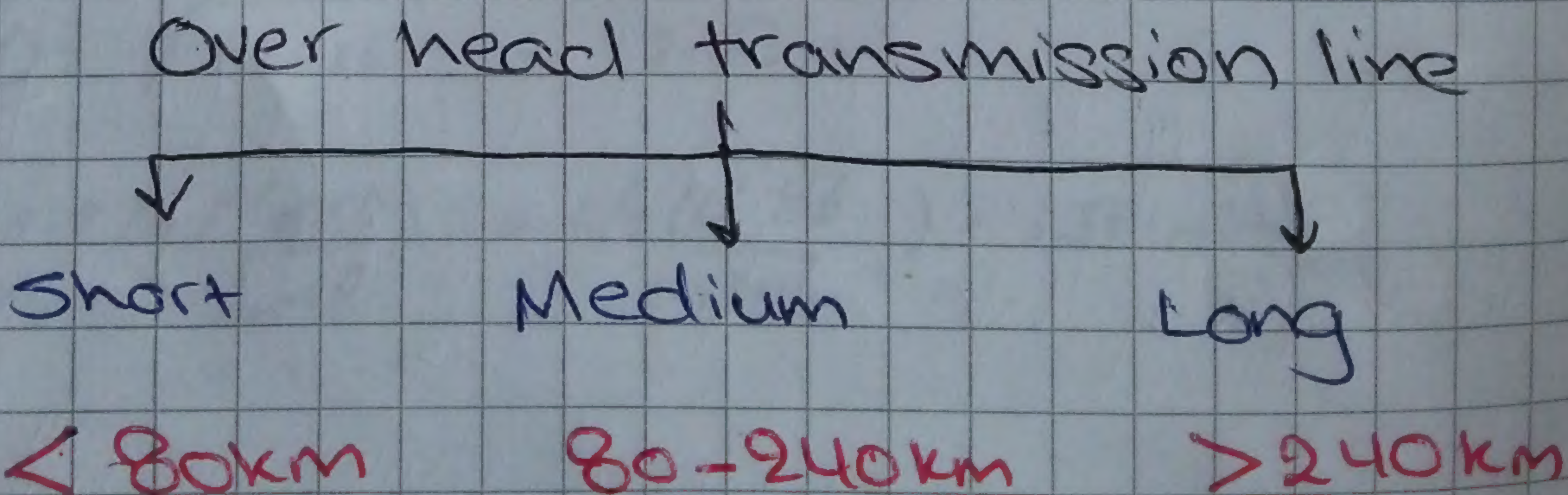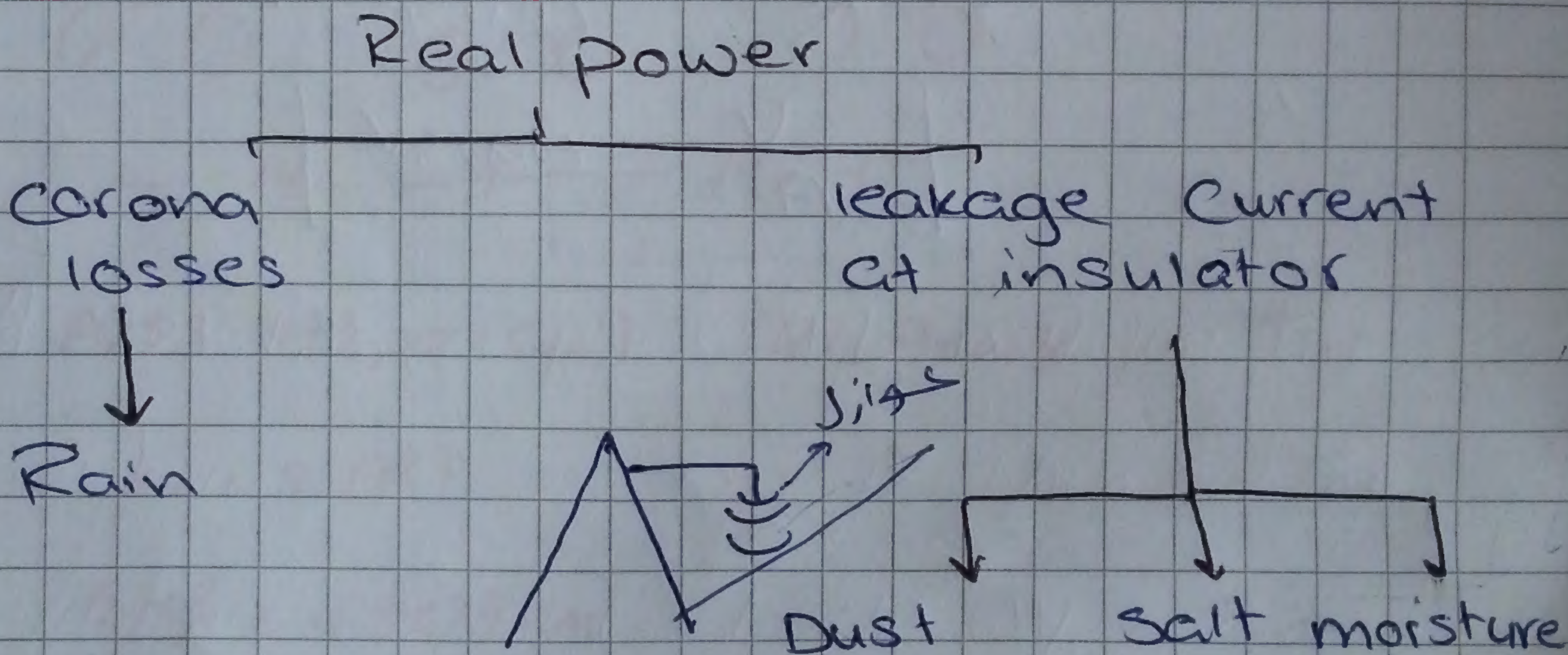

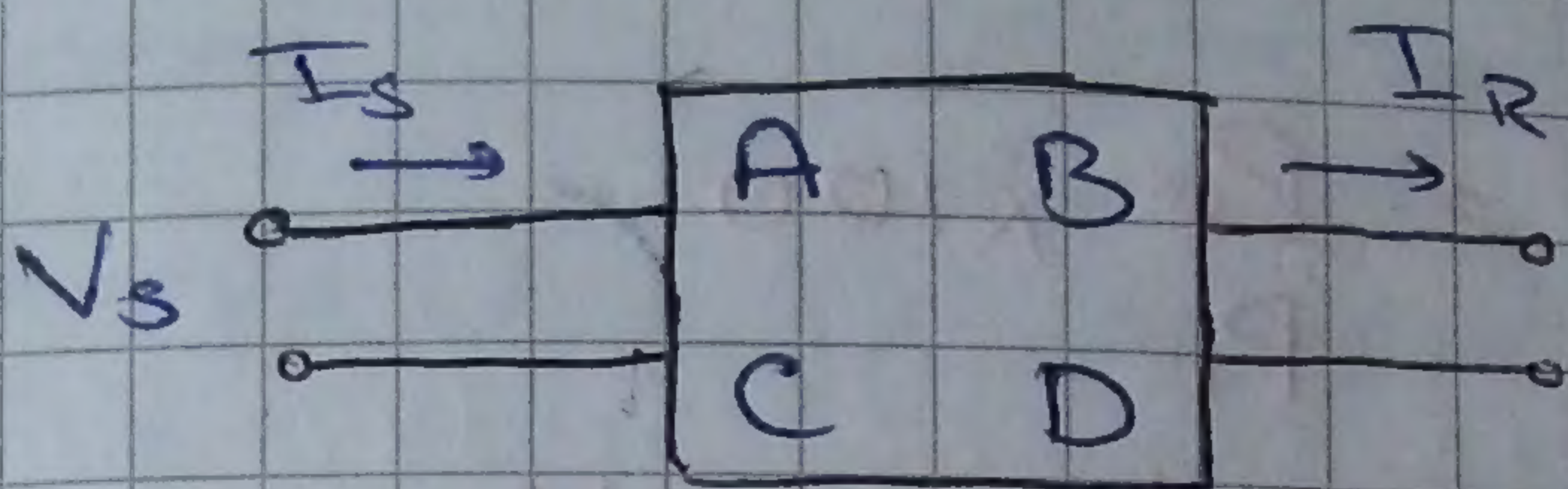

Line Parameters

$$V_s = A V_R + B I_R$$

$$I_s = C V_R + D I_R$$


$V_s \triangleq$ sending voltage

$I_s \triangleq$ sending current

$V_R \triangleq$ receiving voltage

$I_R \triangleq$ receiving current

Short line model

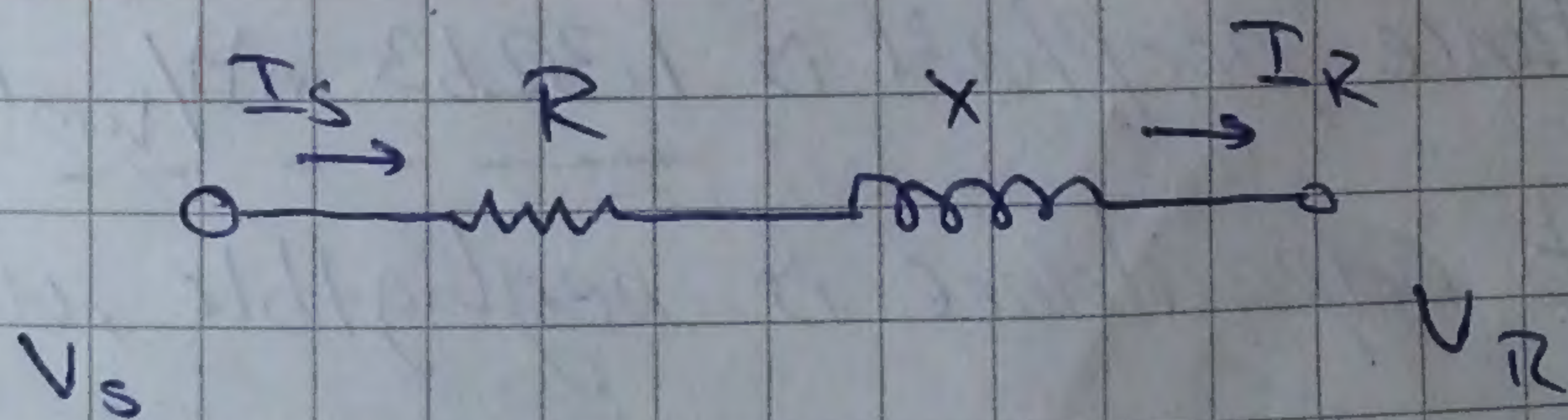

phase to neutral

$$Z = R + jX$$

$$V_s = A V_R + B I_R$$

$$V_s = I_s V_R + Z I_R$$

$$I_s = [0] V_R + [1] I_R$$

$$A = 1 \quad B = Z$$

$$C = 0 \quad D = 1$$

$$\eta = \frac{P_o}{P_i} \times 100$$

$$\%VR = \frac{V_{R(NL)} - V_{R(FL)}}{V_{R(FL)}} \times 100$$

At NO load $I_R = 0$

$$V_s = A V_{R(NL)} + B \cancel{I_R}$$

$$\left[V_{R(NL)} = \frac{V_s}{A} \right]$$

nominal
voltage

$\frac{1}{\sqrt{3}}$

phase to
phase

we use phase to neutral

ie $\frac{V_s}{\sqrt{3}}$

we use phase to neutral

ie $\frac{V_s}{\sqrt{3}}$

we use phase to neutral

ie $\frac{V_s}{\sqrt{3}}$

ex: A 220 kV, three phase T.L is 40 km the

resistance per phase is 0.15 Ω /km and the

inductance per phase is 1.3263 mH/km, the

shunt capacitance is negligible, use the

short model line to find the voltage and

power at sending end and the voltage regulation

and efficiency when the line is supplying a three

phase load of

power
Factor

لارتفاع اداء

a) 381 MVA at 0.8 pf lagging at 220kV

V_R

b) 381 MVA at 0.8 pf leading at 220kV

دائماً لمتقاسم
العكس

$$R = 0.15 \times 40 = 6 \Omega$$

$$X = \omega L = 2\pi(60) \times 1.3263 \times 10^{-3} \times 40 = 20 \Omega$$

$$Z = 6 + j20 = 20.881 \angle 73.3^\circ$$

$$V_R = \frac{220}{\sqrt{3}} = 127 \text{ kV} \angle 0^\circ$$

$$S_{1-\phi} = V_{ph-N} \times I^*$$

$$S_{3\phi} = \sqrt{3} V_{LL} \times I^*$$

$$S_{1-\phi} = \frac{381}{3} = 127 \text{ MVA}$$

$$|I_R| = \frac{127 \times 10^6}{127 \times 10^3} = 1 \text{ kA}$$

$$F_p = \cos \theta \Rightarrow \theta = \cos^{-1}(0.8) = 36.87^\circ$$

$$I_R = 1 \text{ kA} \angle -36.87^\circ$$

$$V_s = A V_R + B I_R$$

$$= 1 + 127 \angle 0 + 20.88 \angle 73.3^\circ \cdot 1 \angle -36.87^\circ$$

$$= 144.33 \text{ kV} \angle 4.93$$

$$|V_s| = \sqrt{3} (144.33) = 250 \text{ kV}$$

$$I_s = I_R = 1 \text{ kA} \angle -36.87^\circ$$

$$S_{SC1\phi} = V_{s1} \cdot I_s^*$$

$$= 144.33 \angle 4.93^\circ \cdot 1 \angle -36.87^\circ$$

$$= 144.33 \angle 41.9^\circ$$

$$S_{3\phi} = 3 S_{1\phi} = 432.99 \text{ MVA} \angle 41.9^\circ$$

$$= \underbrace{322.8}_{P_s} + j \underbrace{288.6}_{Q_s}$$

$$P_R = S_R + P_P$$

$$= 381 \times 0.8 = 304.8 = 304.8 \text{ MW}$$

$$\eta = \frac{304.8}{322.8} \times 100 = 94.4\%$$

$$\%VR = \frac{V_R(NL) - V_R(FL)}{V_R(FL)}$$

$$V_R(NL) = \frac{V_s}{A} - \frac{250}{I} = 250 \text{ kV}$$

$$\%VR = \frac{250 - 220}{220} \times 100 = 13.6\%$$

lecture
10

at the last example

b) 381 MVA at 0.8 power factor leading at 220 kV

$$Z = 6 + j20 \Omega = 20.88 \angle 73.3^\circ$$

$$V_R = \frac{220}{\sqrt{3}} = 127 \text{ kV} \angle 0$$

$$|I_R| = 1 \text{ kA}$$

$$\theta = \cos^{-1}(0.8) = 36.87^\circ$$

$$I_R = 1 \text{ kA} \angle 36.87^\circ$$

$$V_S = 1 \angle 0 + \frac{127}{\text{kV}} \angle 0 + \frac{20.88}{\Omega} \angle 73.3^\circ \times \frac{1}{\text{kA}} \angle 36.87^\circ$$

$$V_S = 121.39 \text{ kV} \angle 9.29^\circ$$

$$\rightarrow |V_{S_{LL}}| = \sqrt{3} (121.39) = 210.26 \text{ kV}$$

$$I_S = I_R = 1 \text{ kA} \angle 36.87^\circ$$

$$S = V_S I_S^*$$

$$= 121.39 \angle 9.29^\circ \times 1 \angle -36.87^\circ$$

$$S = P + jQ$$

$$\begin{aligned} S_{3\phi} &= 3 S_{1\phi} = 364.18 \text{ MVA} \angle -27.58^\circ \\ &= \underbrace{322.8 \text{ MW}}_P - j \underbrace{168.0 \text{ MVAR}}_Q \end{aligned}$$

$$\gamma = \frac{P_o}{P_i} = \frac{P_R}{P_S} \times 100$$

$$\begin{aligned} P_S &= S F_p \\ &= 381 \times 0.8 = 304.8 \text{ MW} \end{aligned}$$

$$\rightarrow \frac{304.8}{322.8} \times 100 = 94.4\%$$

$$V_R(\text{VL}) = 210.26$$

$$VR\% = \frac{210.26 - 220}{220} \times 100 = -4.43\%$$


→ inductive load F_p lagging

$$V_S > V_R$$

→ Capacitive load F_p leading

$$V_S < V_R$$


X

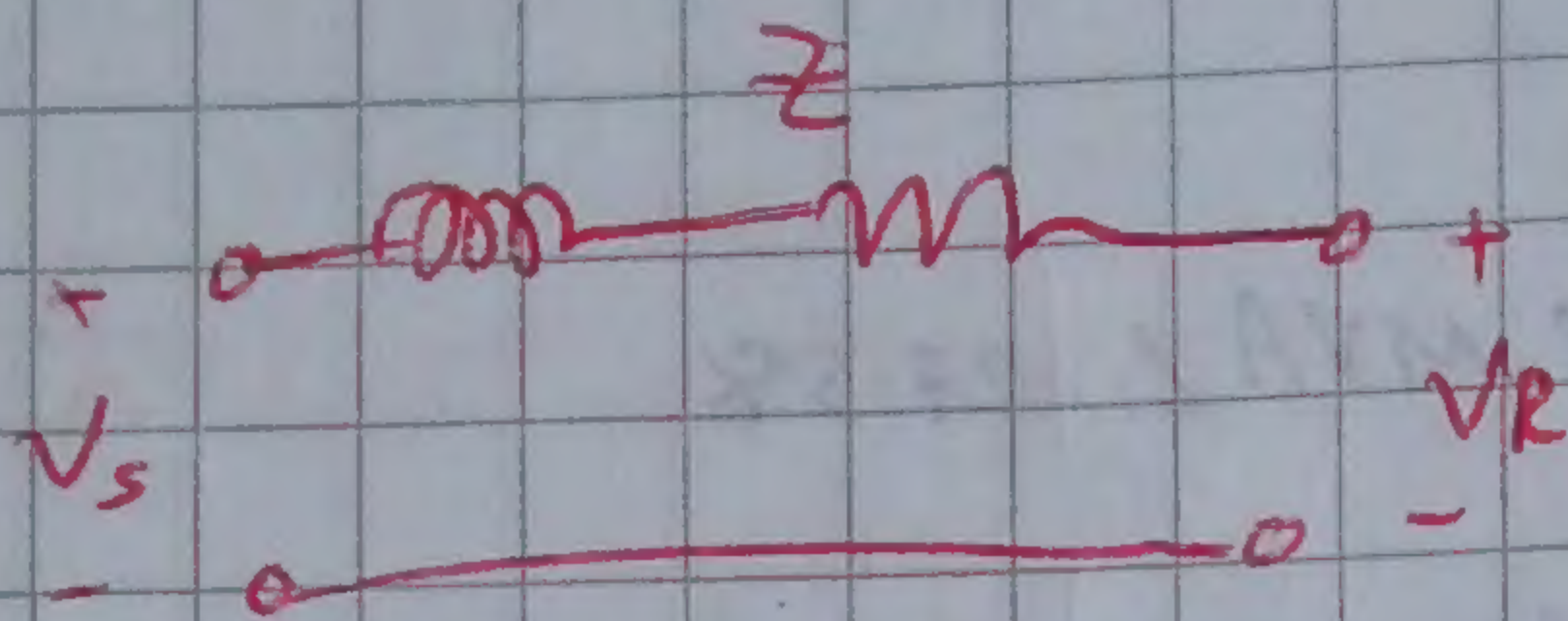


$$V_s = V_R + Z I_R$$

$$= V_R + R I_R + j X I_R$$


lagging

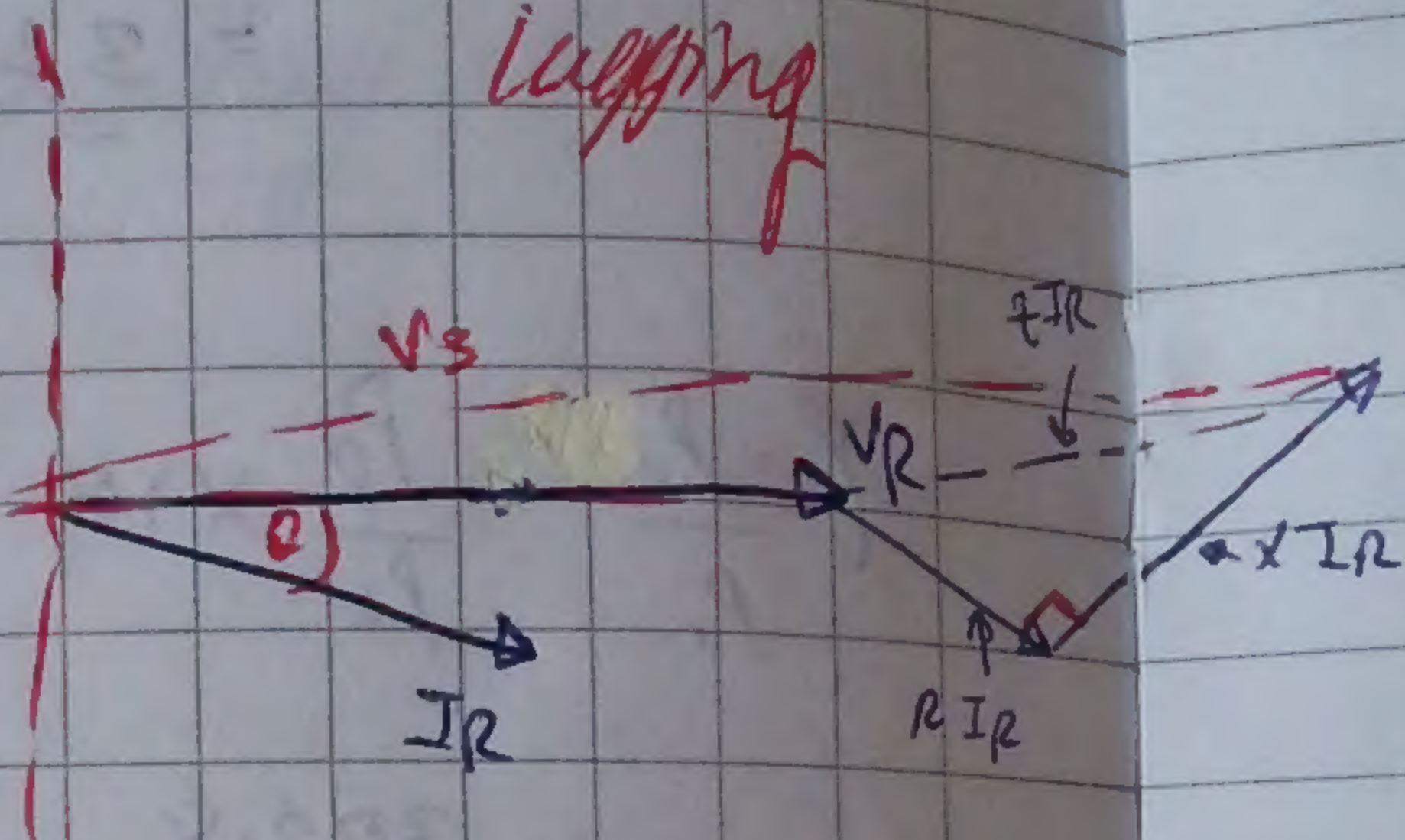


{unity} "in phase"
FP 0

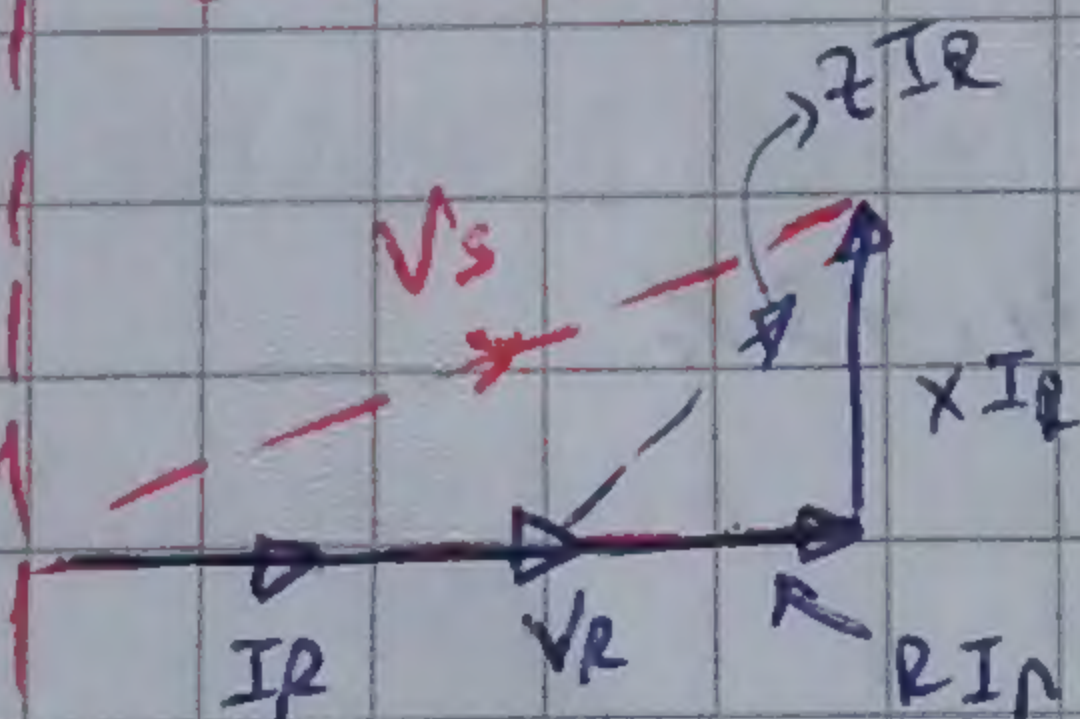

leading

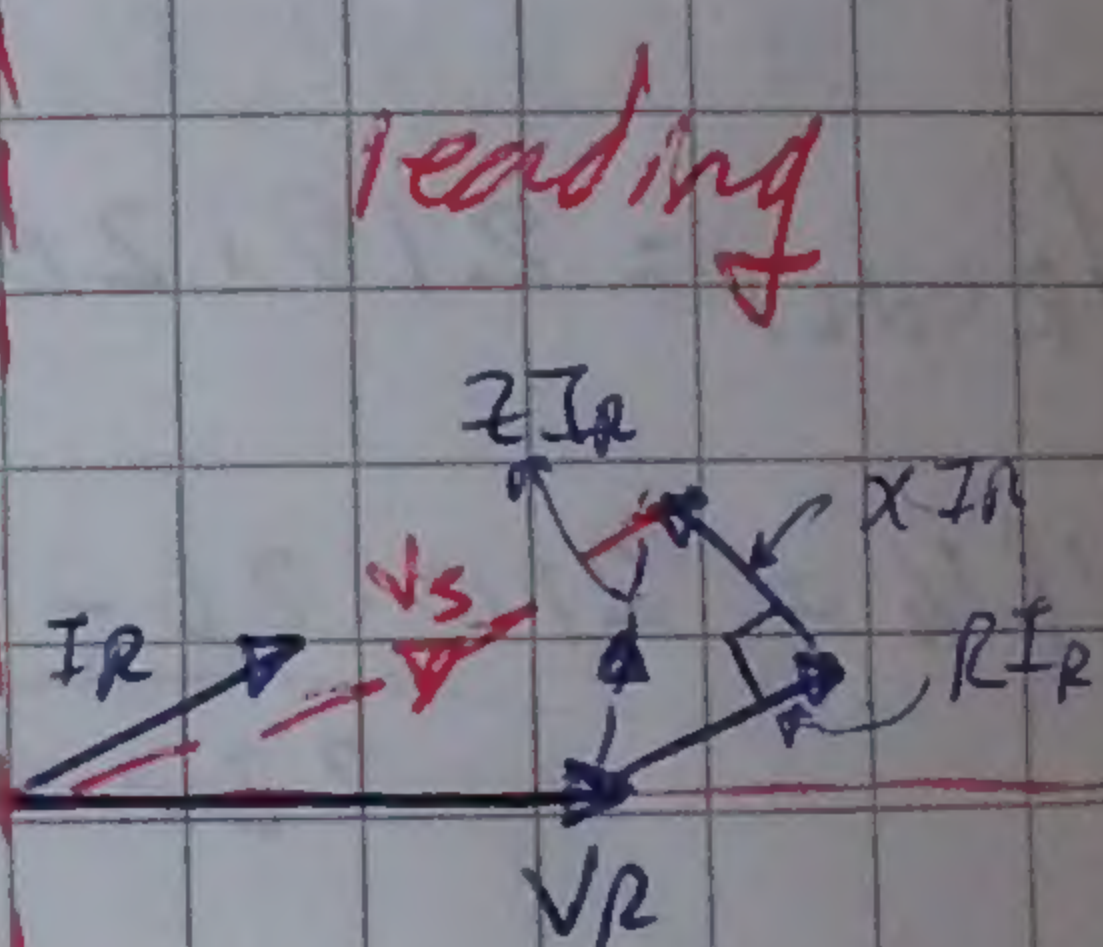

Medium Line Model

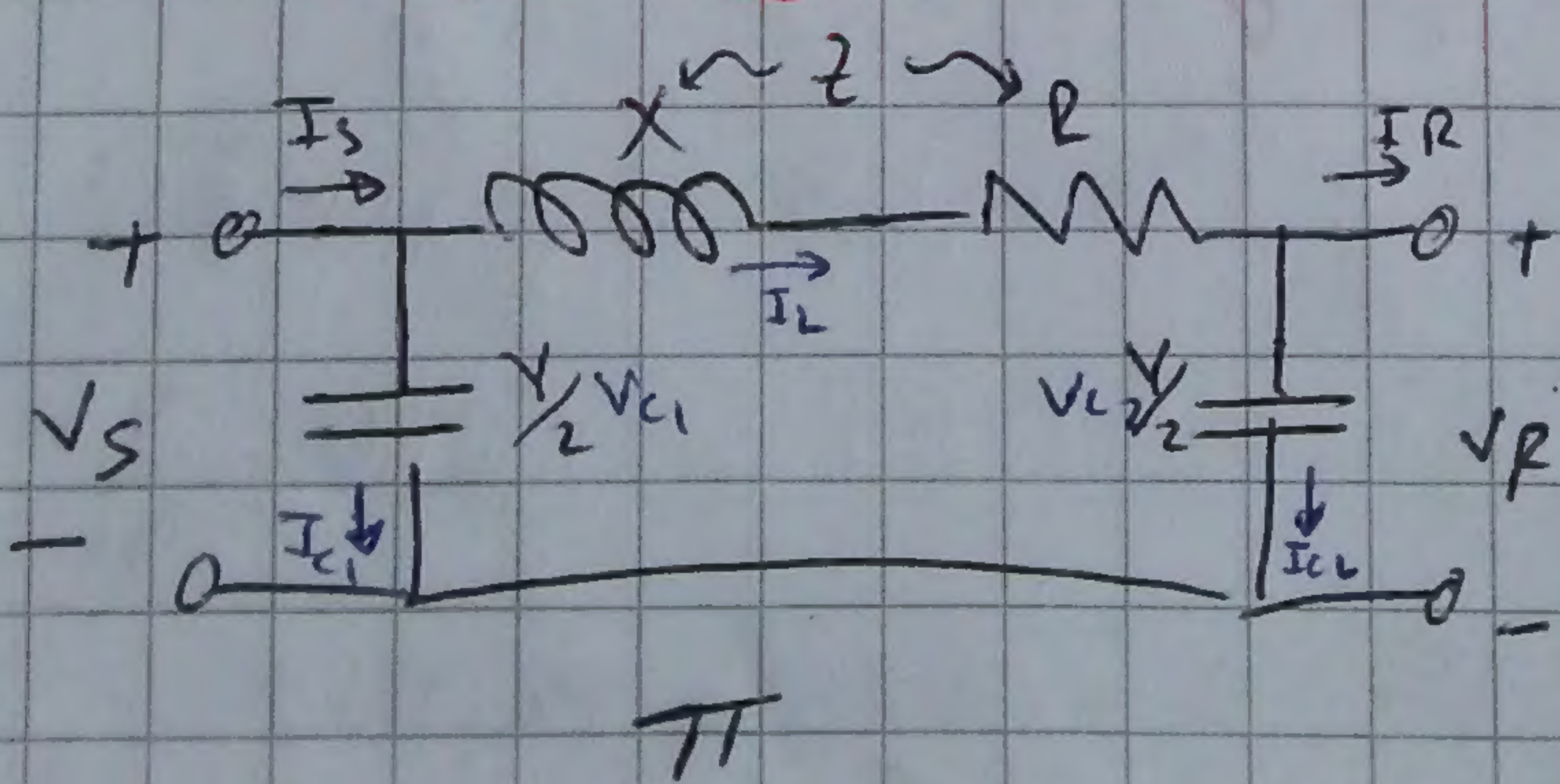

$$\begin{aligned}
 V_s &= V_R + Z I_L \\
 &= V_R + Z (I_{C_2} + I_R) \\
 &= V_R + Z \left(\frac{Y}{2} V_R + I_R \right)
 \end{aligned}$$

$$= V_R + \frac{ZY}{2} V_R + Z I_R$$

$$= \underbrace{\left(1 + \frac{ZY}{2} \right)}_A V_R + \underbrace{Z I_R}_B$$

$$I_s = I_{C_1} + I_L$$


$$= \frac{Y}{2} V_s + (I_{C_2} + I_R)$$

$$= \frac{Y}{2} V_s + \frac{Y}{2} V_R + I_R$$

$$= \frac{Y}{2} \left[V_R + \frac{ZY}{2} V_R + Z I_R \right] + \frac{Y}{2} V_R + I_R$$

$$= Y V_R + \frac{ZY^2}{4} V_R + \frac{ZY}{2} I_R + I_R$$
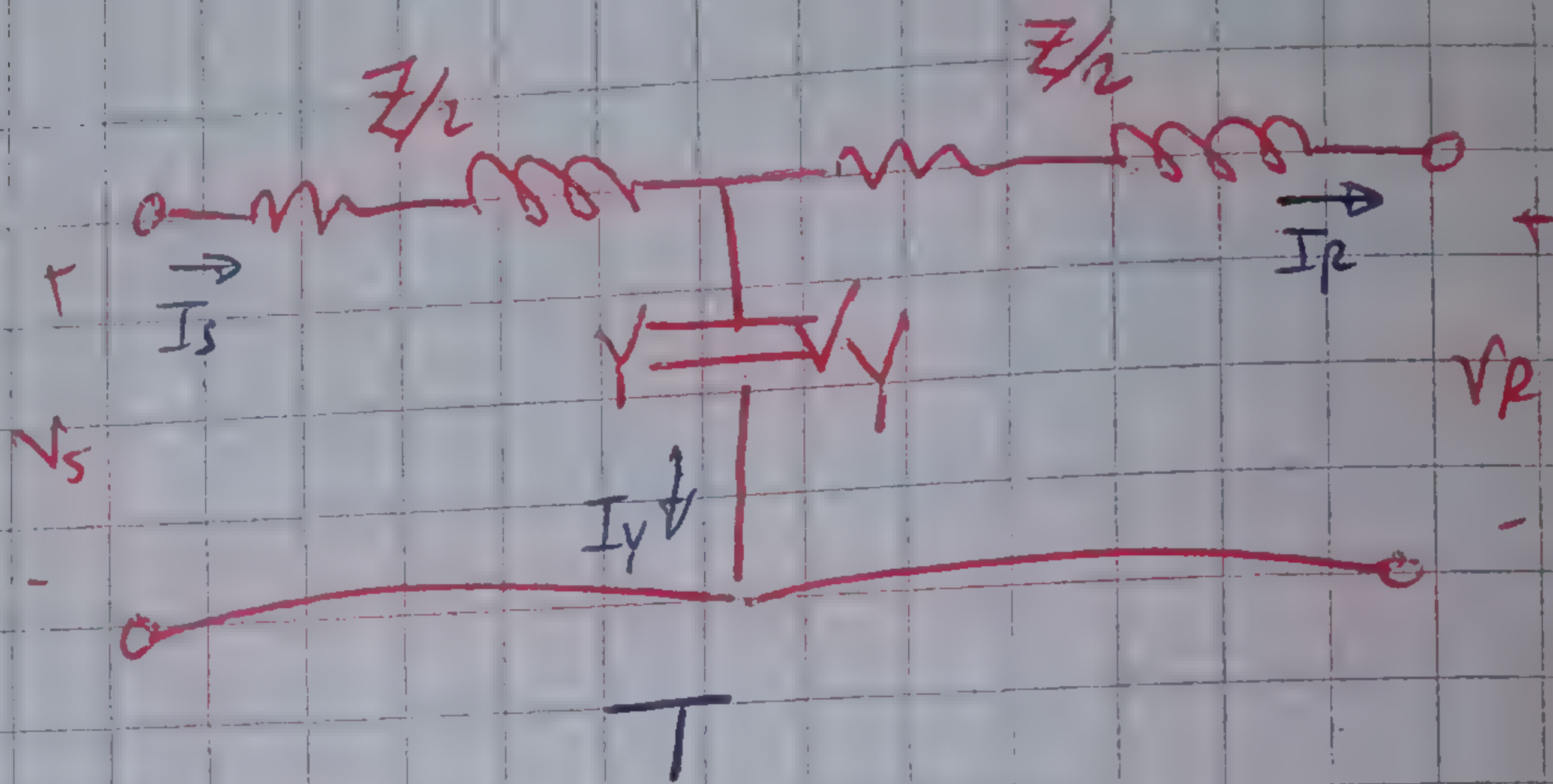
$$I_s = \underbrace{Y \left(1 + \frac{ZY}{4} \right)}_C V_R + \underbrace{\left(1 + \frac{ZY}{2} \right)}_D I_R$$



$$\begin{aligned}
 I_s &= I_R + I_Y \\
 &= I_R + Y V_Y \\
 &= I_R + Y \left[V_R + \frac{Z}{2} I_R \right] \\
 &= Y V_R + I_R + \frac{ZY}{2} I_R
 \end{aligned}$$

$$I_s = Y V_R + (1 + \frac{ZY}{2}) I_R$$

\underline{C}
 \underline{D}

$$V_s = V_Y = \frac{Z}{2} I_s$$

$$= V_R + \frac{Z}{2} I_R + \frac{Z}{2} \left[Y V_R + I_R + \frac{ZY}{2} I_R \right]$$

$$= V_R + \frac{Z}{2} V_R + \frac{Z}{2} I_R + \frac{Z^2 Y}{4} I_R$$

$$= \underbrace{(1 + \frac{ZY}{2})}_{\underline{A}} V_R + \underbrace{Z(1 + \frac{ZY}{2})}_{\underline{B}} I_R$$

✓ Ex 8-


a) Determine the capacitance to neutral in $\mu\text{F}/\text{mi}$
 and the capacitive reactance ^{to neutral} in $\Omega \cdot \text{mi}$

b) If the line is 150 mile long, find the capacitance
 to neutral and the capacitive reactance of the line

From the table $r = \frac{D}{2} = \frac{0.879}{2} =$

$r = 0.4395 \text{ m}$

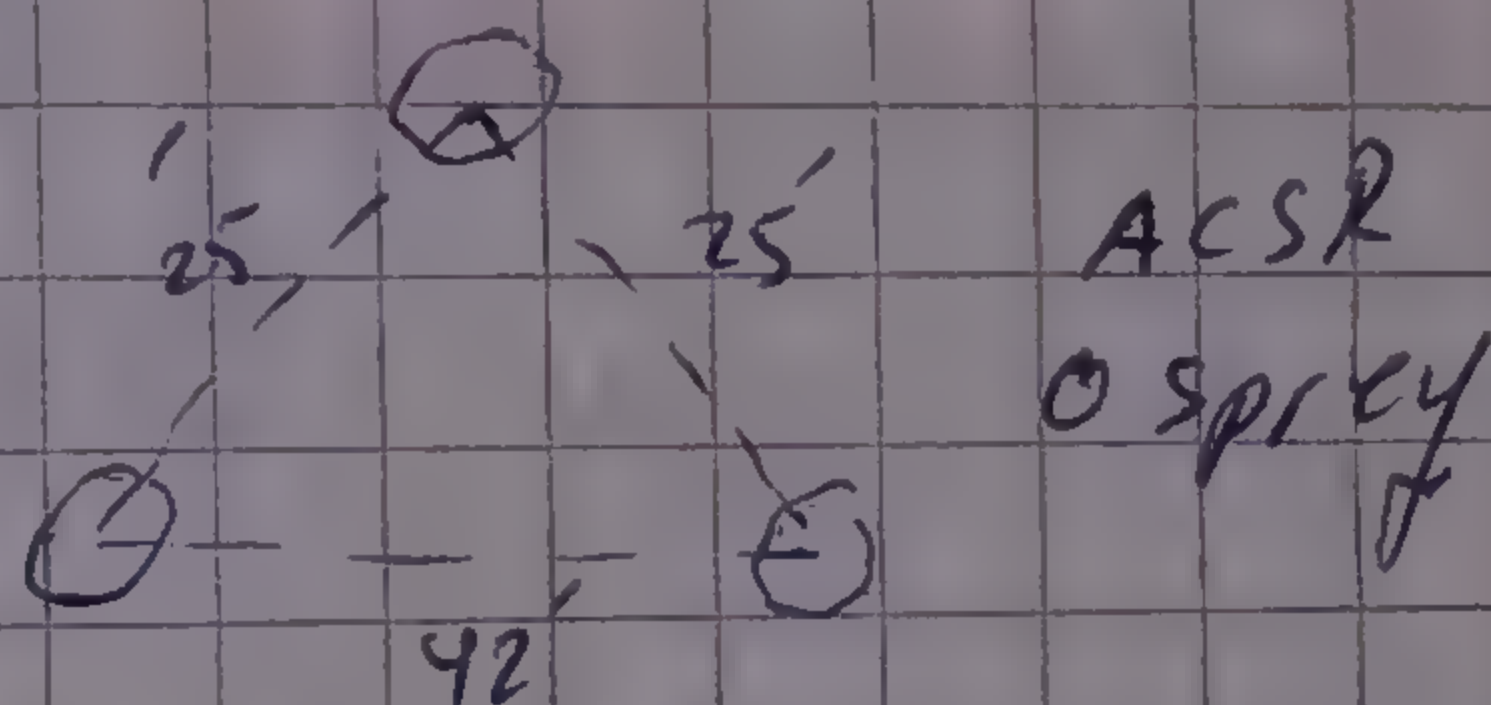$r = \frac{0.4395}{12} = 0.036625 \text{ ft}$



1) $C = \frac{2\pi\epsilon_0}{\ln\left(\frac{D}{r}\right)} = \frac{2\pi\epsilon_0}{\ln\left(\frac{\sqrt{25^2 + 25^2 + 42^2}}{0.036625}\right)} = 8.3 \text{ pF}/\text{m}$

$C = 1609 \times 8.3 \text{ p} = 0.0134 \mu\text{F}/\text{mile}$

$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = 198.5 \text{ k}\Omega \cdot \text{mile}$

2) $C = 2.01 \mu\text{F}$

$X_c = 1.319 \text{ k}\Omega$

lecture

(1)

تابع التكاليف

التي هي دالة في X حيث X هي المسافة

$$X_c = X_a + X_b$$

$$X_a = 0.0981 \text{ Mm. mile}$$

$$X_b = \text{value at GMD} = 29.72$$

حيث أن هذه الدالة لا توجد في الجداول

Interpolation خطية (1)

التي هي دالة في X

$$X_b = 0.06831 \log(d)$$

$$= 0.06831 \log(29.72)$$

$$= 0.1006 \text{ Mm. mile}$$

$$\frac{30 - 29}{0.1007 - 0.0999} = \frac{29.72 - 29}{X - 0.0999} \Rightarrow X = 0.101 \approx 0.0100$$

$$X_c = 0.981 + 0.1006 = 198.7 \text{ k}\Omega \cdot \text{mi}$$

Find the total charge current and the total charge in mega volt amperes

$$I_{ch} = j\omega C V_{\text{phase to neutral}}$$

assume 3 ϕ at 220kV \leftarrow line to line

$$V_{LL} = \sqrt{3} V_{ph-n}$$

$$I_{ch} = \frac{2\pi(60)(2.01\mu) \times 220k}{\sqrt{3}}$$

$$I_{ch} = 96.185 \text{ A}$$

$$S = P + jQ$$

$$Q = \sqrt{3} V I \sin \theta \rightarrow I_{ch}$$

$$= \sqrt{3} (220k) (96.185) = 36.03 \text{ MVAR}$$




$$Q_{ph-n} = V_{ph-n} I \sin \theta$$

$$= \frac{220}{\sqrt{3}} (96.185)$$

$$\Rightarrow Q_{3\phi} = 3 Q_{ph-n}$$



Fe

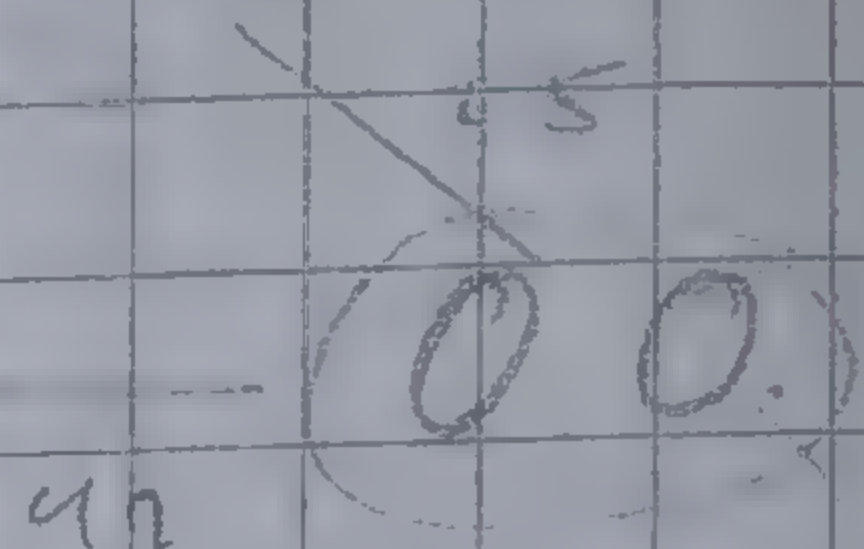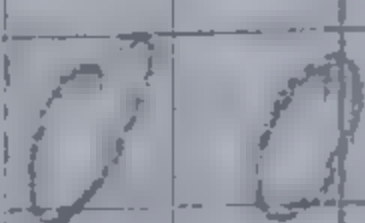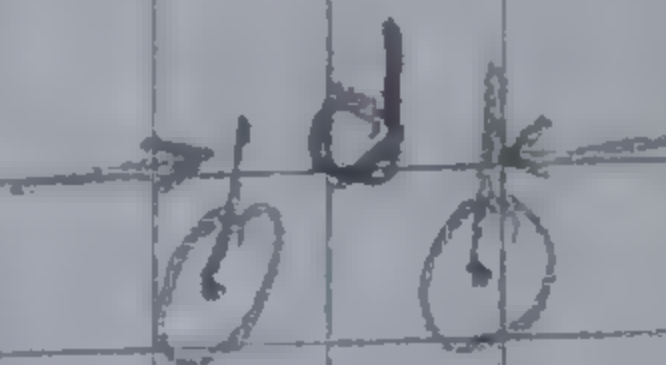

Line to line

$L = 0.1843 \mu H / \text{mile}$
at 500
60 Hz

$$C = \frac{2\pi\epsilon_0}{\ln\left(\frac{GMD}{GMR}\right)}$$

$GMR_c = r$
 $\sqrt{r \times d}$
 $\sqrt[3]{r d^2}$

1 ✓ and
2
3


Capacitance in double circuit (two x one)
C' C



الترتيب يختلف من سلك إلى سلك
inductance

lecture
(12)

Long Line Model :-

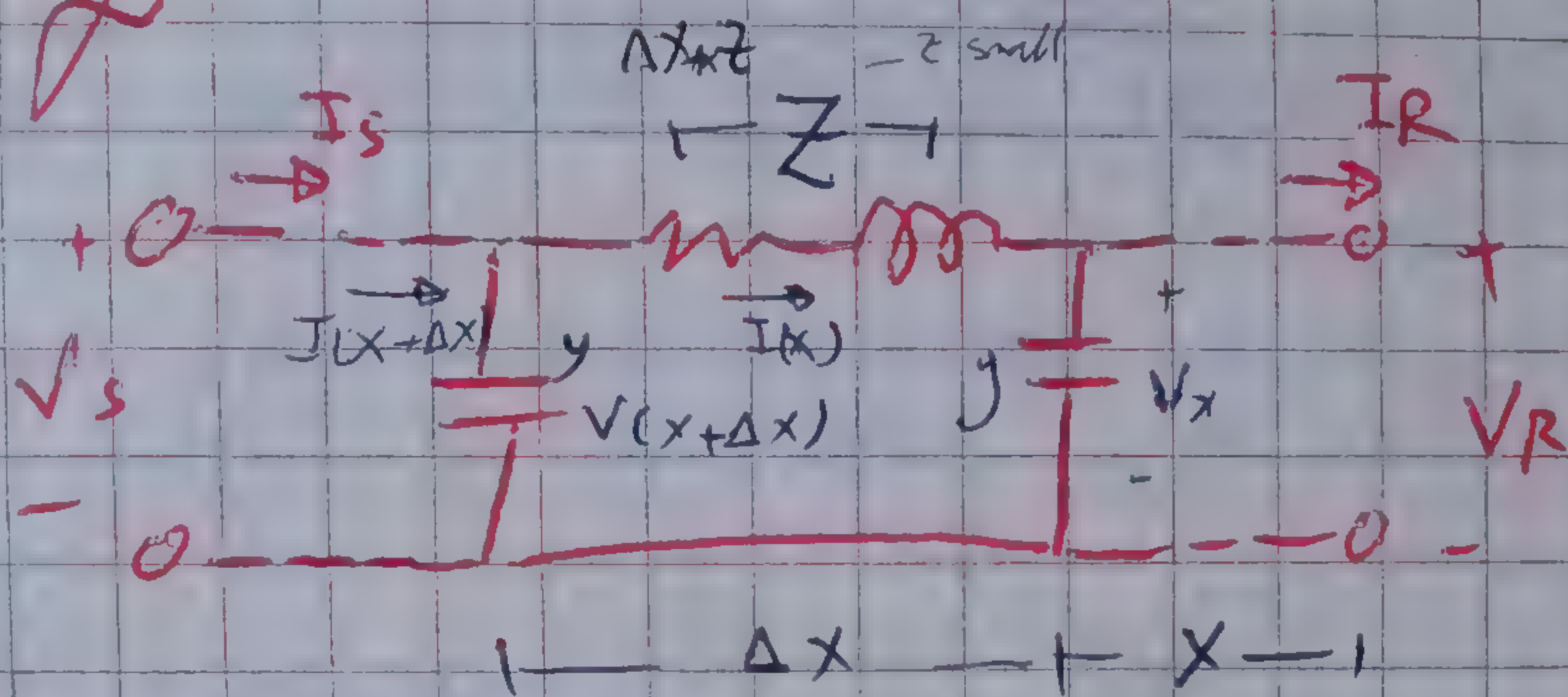

z small

Z = series impedance / unit length

y = shunt admittance

$$V(x + \Delta x) = V(x) + \Delta x \cdot z \cdot I(x)$$

$$z \cdot I(x) = \frac{V(x + \Delta x) - V(x)}{\Delta x}$$

$$\Delta x \rightarrow 0$$

$$\frac{dV(x)}{dx} = -z \cdot I(x) \quad \text{--- (1)}$$

$$I(x + \Delta x) = I(x) + \Delta x \cdot y \cdot V(x + \Delta x)$$

$$\frac{I(x + \Delta x) - I(x)}{\Delta x} = y \cdot V(x + \Delta x)$$

$$\Delta x \rightarrow 0$$

$$\frac{dI(x)}{dx} = \gamma V(x) \quad \text{--- (2)}$$

diff eq (1)

$$\frac{d^2 V(x)}{dx^2} = \gamma \frac{dI(x)}{dx} \quad \text{--- (3)}$$

Sub (3) in (2)

$$\frac{d^2 V(x)}{dx^2} = (\gamma^2 V(x))$$

$$\textcircled{1} \text{ --- } \frac{d^2 V(x)}{dx^2} - \gamma^2 V(x) = 0 \quad \text{diff equation in order 2}$$

$$V(x) = A_1 e^{\gamma x} + A_2 e^{-\gamma x}$$

$\gamma = \sqrt{\gamma' \gamma''} \equiv \text{propagation constant}$

$$\gamma = \alpha + j\beta$$

α
attenuation
constant

β
phase constant

$$I(x) = \frac{1}{Z} \frac{dV(x)}{dx}$$

$$= \frac{1}{Z} [A_1 e^{\gamma x} - A_2 e^{-\gamma x}] \gamma$$

$$= \frac{\sqrt{Y Z}}{Z} [\quad]$$

$$= \sqrt{\frac{Y}{Z}} [\quad]$$

$$Z_c = \sqrt{\frac{Z}{Y}} \quad \text{characteristic impedance}$$

$$I(x) = \frac{1}{Z_c} [A_1 e^{\gamma x} - A_2 e^{-\gamma x}] \quad - (2)$$

To find A_1 and A_2

$$\text{at } x=0 \Rightarrow V(x) = V_R, \quad I(x) = I_R$$

$$V_R = A_1 + A_2$$

$$I_R = \frac{1}{Z_c} (A_1 - A_2)$$

$$\Rightarrow A_1 = \frac{V_R + Z_c I_R}{2}, \quad A_2 = \frac{V_R - Z_c I_R}{2}$$

Long model more accurate than medium model
 def medium = typical line long = 100 km or more

$$V(x) = \left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x} + \left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x}$$

$$I(x) = \frac{1}{Z_c} \left[\left(\frac{V_R + Z_c I_R}{2} \right) e^{\gamma x} - \left(\frac{V_R - Z_c I_R}{2} \right) e^{-\gamma x} \right]$$

$$V(x) = \overset{\text{Cosh}}{\left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right)} V_R + Z_c \overset{\text{sinh}}{\left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right)} I_R$$

$$I(x) = \frac{1}{Z_c} \underset{\text{sinh}}{\left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right)} V_R + \underset{\text{cosh}}{\left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right)} I_R$$

Line length = $L = x$

$$V(L) = V_s, \quad I(L) = I_s$$

$$V_s = \overset{A}{\cosh(\gamma L)} V_R + \overset{B}{Z_c \sinh(\gamma L)} I_R$$

$$I_s = \underset{C}{\frac{1}{Z_c} \sinh(\gamma L)} V_R + \underset{D}{\cosh(\gamma L)} I_R$$

$$(AD - BC = 1)$$

$$\bar{Z} = Z_c \sinh(\gamma l)$$

$$= \frac{\sqrt{Z}}{\sqrt{Y}} \times \frac{\sqrt{Z}}{\sqrt{Y}} \times \frac{1}{1} \sinh(\gamma l)$$

$$= \frac{Z l}{\gamma l} \sinh(\gamma l)$$

$$\bar{Z} = \frac{Z}{\gamma l} \sinh(\gamma l)$$

$$1 + \frac{Z \bar{Y}}{2} = \cosh(\gamma l)$$

$$1 + \frac{\bar{Y} Z_c \sinh(\gamma l)}{2} = \cosh(\gamma l)$$

$$\frac{\bar{Y}}{2} = \frac{\cosh(\gamma l) - 1}{Z_c \sinh(\gamma l)}$$

$$= \frac{1}{Z_c} \tanh\left(\frac{\gamma l}{2}\right)$$

$$\boxed{\frac{\bar{Y}}{2} = \frac{Y}{2} \frac{\tanh(\gamma l/2)}{(\gamma l/2)}}$$

$$\frac{2\pi}{\omega} = \frac{2\pi}{2\pi f}$$

Voltage and current waves :-

lecture
(13)

velocity of propagation $v = \frac{\omega}{\beta}$

wave length $\lambda = \frac{2\pi}{\beta} = v/f$

Ex 8 - A single cat 60Hz T.L, is 370km

(230 mile) long. The conductors are Rook

with flat horizontal, spacing 7.25m (23.8 ft)

between conductors, the load on the line is

125 MW at 215 kV with 100% PF

Find the voltage, current and power at

sending end and % V.R of the line, Also

determine the wave length and velocity of

propagation of the line

$$z = \frac{\Omega}{\text{unit length}}$$


$$Z = \Omega$$

$$\gamma = \alpha + j\beta = \sqrt{zy} \Rightarrow \gamma l = \sqrt{zy}$$

$$z = r + jX_L$$

From table r (AC at 50°C)
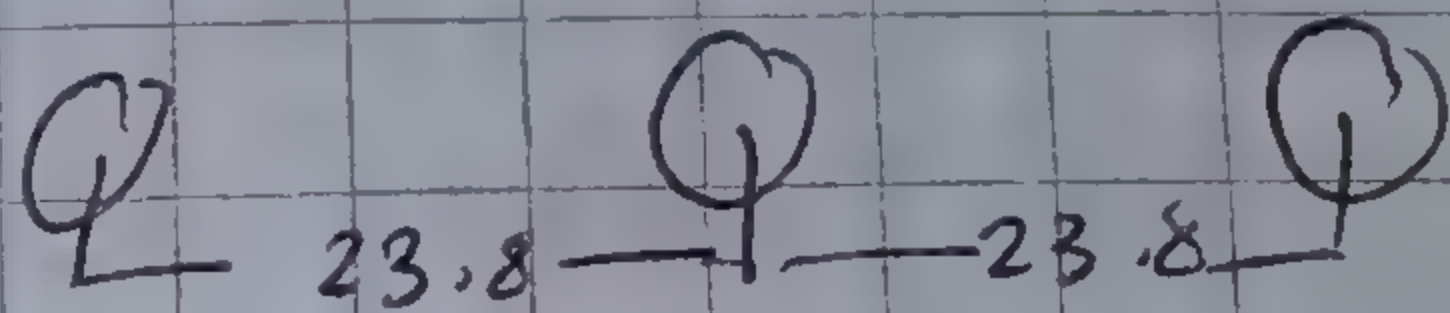
$$r = 0.1603 \text{ } \Omega/\text{mile}$$



$$X_L = X_a + X_d \xrightarrow{\text{For GMD}} = 0.415 + 0.4127 = 0.8277 \text{ } \Omega/\text{mile}$$

$$\text{GMD} = \sqrt{23.8 \times 23.8 \times (23.8 \times 2)} = 30 \text{ ft}$$

$$Z = 0.1603 + j0.8277 = 0.8431 \angle 79.04^\circ \text{ } \Omega/\text{mile}$$

Zero S, L, C \rightarrow

$$y = g + jb \Rightarrow y = jb = j \frac{1}{X_c} = j \frac{1}{X_a + X_d}$$

$$y = j \frac{1}{0.0950 + 0.1009}$$

$$X_a \text{ From table} = 0.0950 \text{ M}\Omega/\text{mi}$$

$$X_d = 0.1009 \text{ M}\Omega/\text{mile}$$

$$y = 5.105 \times 10^{-6} \angle 90^\circ \text{ S/mile}$$

تحت الجذر الزوايا تنجمع وتنفك على 2

$$\gamma l = l \sqrt{zy} = 230 \sqrt{0.8431 \times 5.105 \times 10^{-6}} \angle \frac{79.04 + 90}{2}$$

$$= 0.4772 \angle 84.52^\circ = 0.456 + j0.475$$

$$\gamma l = \underbrace{0.456}_{\gamma l} + j \underbrace{0.475}_{\beta l = \text{rad}}$$

rad \rightarrow degree

$$\cosh(\gamma l) = \frac{e^{\gamma l} + e^{-\gamma l}}{2}$$

$$\frac{0.475 \times 180}{\pi}$$

$$= 27.22^\circ$$

$$= \frac{1}{2} e^{\alpha l} \angle \beta l + \frac{1}{2} e^{-\alpha l} \angle -\beta l$$

$$= \frac{1}{2} e^{0.456} \angle 27.22^\circ + \frac{1}{2} e^{-0.456} \angle -27.22^\circ$$

$$\sinh(\gamma l) = \frac{e^{\gamma l} - e^{-\gamma l}}{2} = 0.8902 + j0.0209 = 0.8904 \angle 1.34^\circ$$

$$\sinh(\gamma l) = \frac{1}{2} e^{\alpha l} \angle \beta l - \frac{1}{2} e^{-\alpha l} \angle -\beta l$$

$$= 0.0406 + j0.4579 = 0.4597 \angle 84.93^\circ$$

$$V_R = \frac{215}{\sqrt{3}} \angle 0^\circ = 124.13 \angle 0^\circ \text{ kV}$$

$$P_{3\phi} = \sqrt{3} I_L V_L \text{ pf}$$

$$I = \frac{125 \times 10^6}{\sqrt{3} \times 215 \times 10^3 \times 4} = 335.7 \text{ A } \angle 0^\circ$$

$$Z_c = \sqrt{\frac{r}{y}} = \sqrt{\frac{0.8431}{5.105 \times 10^{-6}}} \angle \frac{79.04 - 90}{2}$$

$$Z_c = 406.4 \angle -5.46 \Omega$$

$$V_s = (0.8907 \angle 1.34^\circ) \left[\frac{124.13 \angle 0^\circ}{\times 10^3} \right] + (406.4 \angle -5.84^\circ) \left[\frac{0.4597 \angle 84.93^\circ}{\times 10^3} \right]$$

$$V_s = 137.86 \angle 27.69 \text{ kV} \quad [335.7 \angle 0^\circ] \quad I_R$$

$$|V_s|_{L.L} = 137.86 \sqrt{3} = 238.8 \text{ kV}$$

$$I_s = \frac{1}{406.4 \angle -5.84^\circ} * 0.4597 \angle 84.93^\circ + 124.13 \angle 0^\circ * 0.8907 \angle 1.34^\circ + 0.3357 \angle 0^\circ$$

$$= 332.31 \angle 26.33 \text{ A}$$

$$P_s = \sqrt{3} V_s I_s \text{ Pf}_s$$

$$\text{Pf}_s = \cos(27.77 - 26.33) = 0.9997 \approx 1.0$$

$$P_s = \sqrt{3} \left(\frac{238.8}{\text{kV}} \right) \left(\frac{0.3323}{\text{kA}} \right) (1) = 137.14 \text{ MW}$$

$$\% VR = \frac{V_{R(NL)} - V_{R(FL)}}{V_{R(FL)}} \times 100$$

$$V_{R(NL)} = \frac{V_s}{A} = \frac{137.86}{0.8904} = 154.83 \text{ kV}$$

$$\% VR = \frac{154.83 - 124.13}{124.13} \times 100 = 24.7 \%$$

$$\beta = \frac{0.475}{230} = 0.002065 \text{ rad/mi}$$

$$v = \frac{\omega}{\beta} = \frac{2\pi(60)}{0.002065} = 182580 \text{ mi/sec}$$

$$\lambda = \frac{v}{f} = \frac{182580}{60} = 3043 \text{ mile}$$

Ex 8 Find the equivalent π circuit for the line described in previous example and compare it with the normal π circuit

$$\bar{Z} = Z_L \sinh(\gamma L) = (406.41 \angle -5.48^\circ)(0.4597 \angle 84.93^\circ)$$

$$\bar{Z} = 186.82 \angle 79.45^\circ \Omega$$

$$\bar{Y}_{\frac{1}{2}} = \frac{1}{Z_0} \tanh\left(\frac{\gamma l}{2}\right) = \frac{1}{Z_0} \cdot \frac{\cosh(\gamma l) - 1}{\sinh(\gamma l)} = \bar{Z}$$

$$= \frac{(0.8902 + j0.0209) - 1}{186.82 \angle 79.45^\circ} = 0.000599 \angle 89.82^\circ$$

$$Z = Z_l = 0.8431 \angle 79.04^\circ + 230 = 193.9 \angle 79.04^\circ$$

$$\frac{Y}{2} = \frac{Y_{xl}}{2} = \frac{5.105 \times 10^{-6} \angle 90^\circ \times 230}{2}$$

$$= 0.000587 \angle 90^\circ$$

$$Z > \bar{Z} \quad \text{by } 3.8\%$$

$$\frac{Y}{2} < \bar{Y}_{\frac{1}{2}} \quad \text{by } 2\%$$

the
are

84.93°

lecture
(14)

$$V(x) = \cosh(\gamma x) V_R + Z_c \sinh(\gamma x) I_R$$

$$I(x) = \frac{1}{Z_c} \sinh(\gamma x) V_R + \cosh(\gamma x) I_R$$

$$v = \frac{\omega}{\beta} \quad , \quad \lambda = \frac{v}{f}$$

Lossless line :

$$r=0 \quad , \quad g=0$$

$$Z = r + j\omega L \quad , \quad Y = g + j\omega C$$

$$\gamma = \alpha + j\beta \quad \text{with } r=0 \text{ and } g=0 \Rightarrow \gamma = j\beta$$

$$\gamma = \sqrt{ZY} = \sqrt{j\omega L + j\omega C} = j\omega \sqrt{LC}$$

$$\beta = \omega \sqrt{LC}$$

$$Z_c = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{L}{C}}$$

→ in loss line \equiv pure resistance

$$v = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$\lambda = \frac{v}{f} = \frac{1}{f\sqrt{\epsilon\epsilon_0}}$$

Neglecting Internal Flux :

$$GMR_L = GMR_c$$

$$L = 2 \times 10^{-7} \ln\left(\frac{GMD}{GMR}\right)$$

$$C = \frac{2\pi\epsilon_0}{\ln\left(\frac{GMD}{GMR}\right)}$$

$$v = \frac{1}{\sqrt{\epsilon\epsilon_0}} = \frac{1}{\sqrt{\mu_0\epsilon_0}} = 3 \times 10^8 \text{ m/s} \quad \text{speed of light}$$

$$\lambda = \frac{1}{f\sqrt{\epsilon\epsilon_0}} = \frac{1}{f\sqrt{\mu_0\epsilon_0}} = 5000 \text{ km}$$

60 Hz

$$Z_c = \sqrt{\frac{L}{C}} = \frac{1}{2\pi} \sqrt{\frac{\mu_0}{\epsilon_0}} \ln\left(\frac{GMD}{GMR_c}\right)$$

$$= 60 \ln\left(\frac{GMD}{GMR_c}\right)$$

$$\cosh(\gamma x) = \cosh(j\beta x) = \cos(\beta x)$$

$$\sinh(\gamma x) = \sinh(j\beta x) = j \sin(\beta x)$$

$Z_c \equiv \text{charact impedance} \equiv \text{surge impedance}$


$$V(x) = \cos(\beta x) V_R + j Z_c \sin(\beta x) I_R$$

$$I(x) = j \frac{1}{Z_c} \sin(\beta x) V_R + \cos(\beta x) I_R$$

For typical T.L Z_c varies from 700 Ω

for 69 kV — 250 Ω for double cat 765 kV

Surge Impedance Loading :

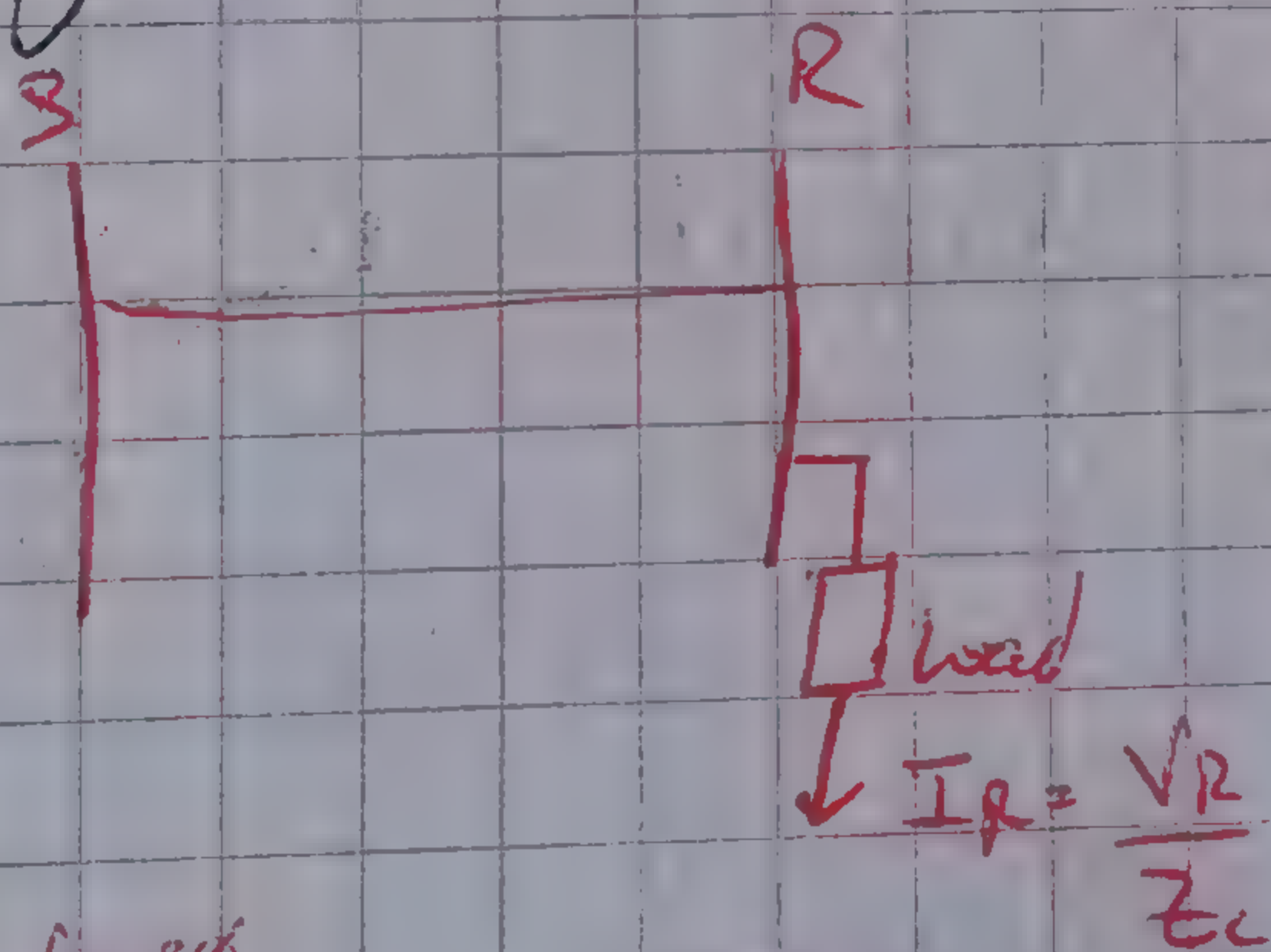

for 3 ϕ ph-v

$$SIL = 3 V_R I_R^*$$
$$= \frac{3 V_R^2}{Z_c}$$

$$SIL = 3 \left(\frac{V_{r.L.L}}{\sqrt{3}} \right)^2 \frac{1}{Z_c} = \frac{V_{r.L.L}^2}{Z_c} \text{ MW}$$

in the example of last lecture

using lossless assumption

$$L = 230 \text{ mi}, \quad Z = 0.1603 + j0.8277$$

$$V_r = 124.13 \angle 0 \text{ kV}, \quad Y = 5.105 \times 10^{-6} \text{ S/mi}$$

$$I_r = 335.7 \angle 0 \text{ A}$$

$$Z = jX_L \Rightarrow X_L = 0.8277 \Rightarrow L = \frac{0.8277}{2\pi f}$$

$$L = 2.1955 \text{ mH/mile}$$


$$5.105 \times 10^{-6} = \omega C \Rightarrow C = 1.35 \times 10^{-8} \text{ F/mile}$$

$$\gamma = \sqrt{ZC} = \sqrt{j\omega L C} = j 2.03 \times 10^{-3}$$

$$\beta l = 2.03 \times 10^{-3} \text{ rad/mile} \times 230 = \beta l = 4.669 \times 10^{-4} \text{ rad/mile}$$

$$Z_0 = \sqrt{\frac{L}{C}} = 403.27 \Omega$$

$$V_{r.L.L} = 124.12563$$

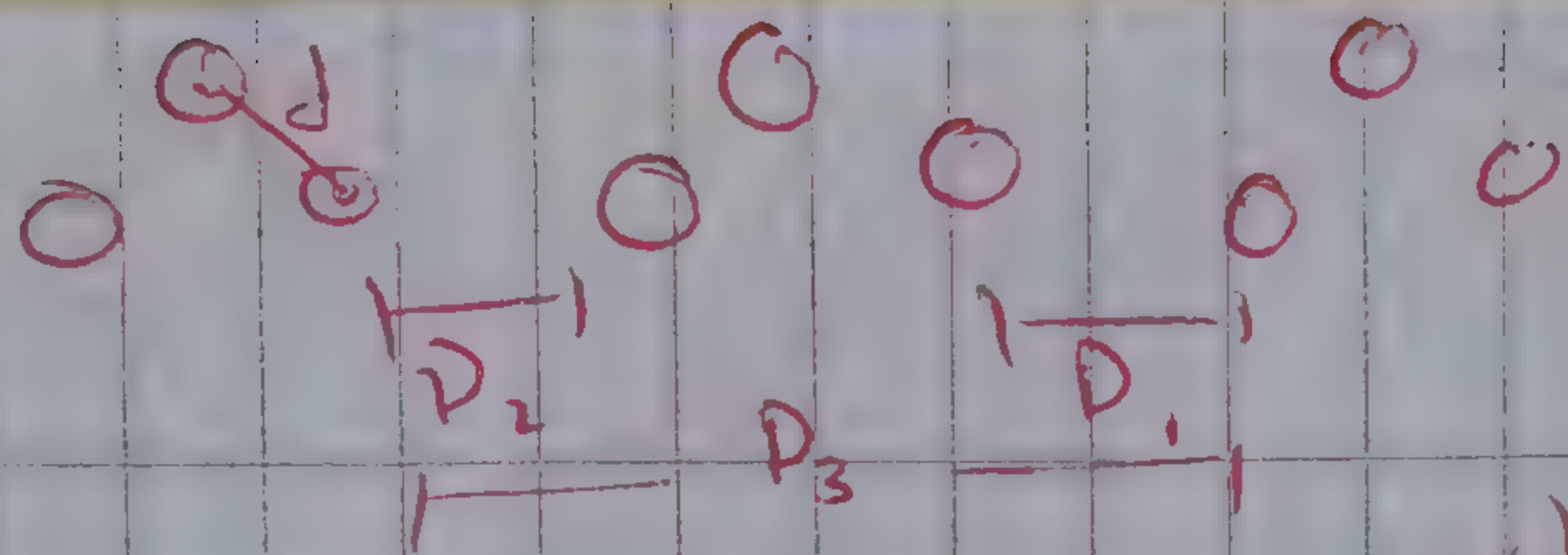


lecture
(15)

$$GMD = \sqrt[3]{D_1 D_2 D_3}$$

$$L_{MR} = \sqrt{GMR \times d^2}$$

$$L = 2 \times 10^{-7} \ln \left(\frac{GMD}{GMR} \right)$$

Complex power flow Through T.L :-

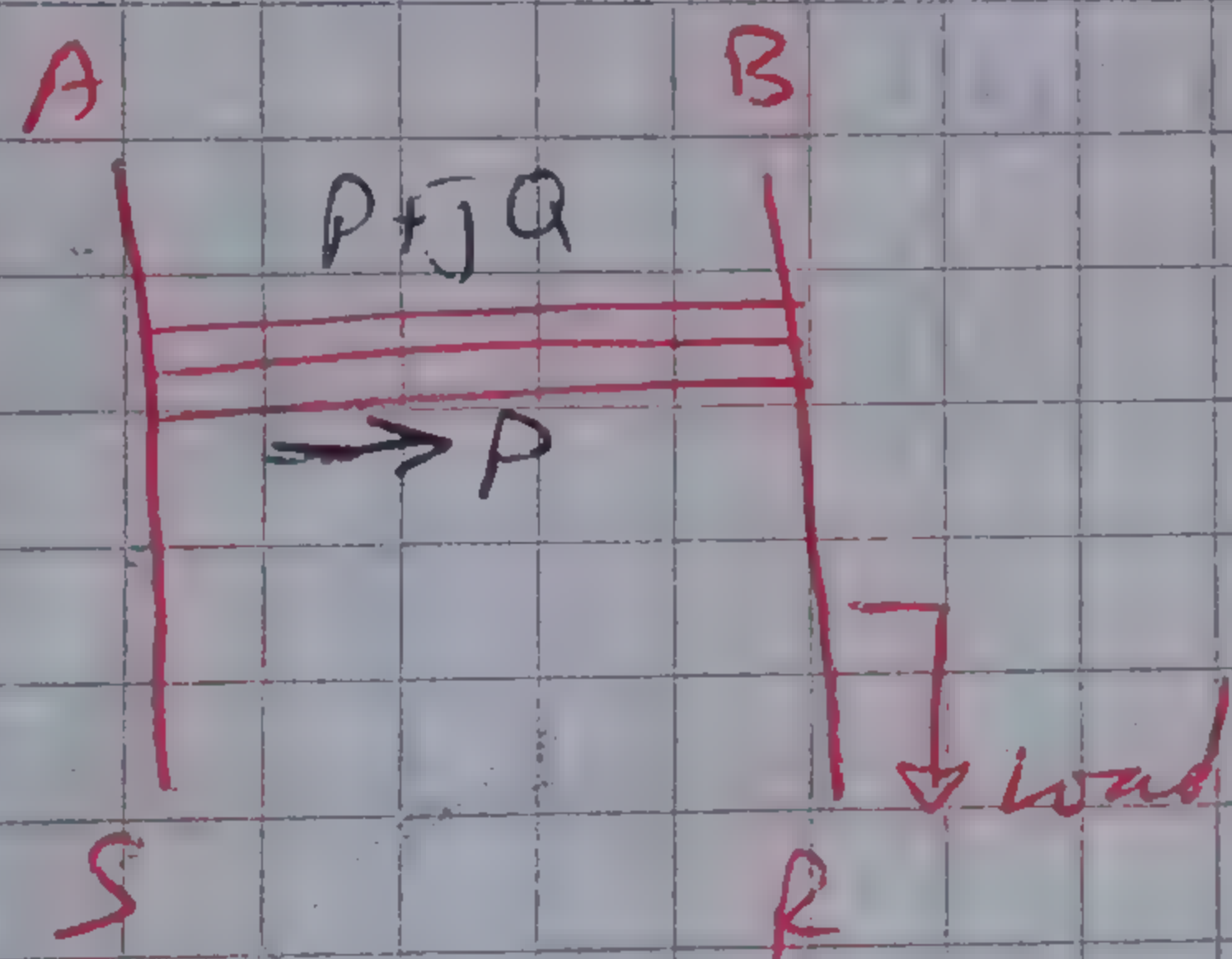

$$S = P + jQ$$

$$S = A \angle \theta$$

$$P = A \cos \theta$$

$$Q = A \sin \theta$$

(i)

$$V_s = A V_r + B I_r$$

$$A = |A| \angle \theta_A$$

$$B = |B| \angle \theta_B$$

$$V_r = |V_r| \angle 0^\circ$$

$$V_s = |V_s| \angle \delta$$

$$I_r = \frac{|V_s| \angle \delta - (|A| \angle \theta_A) (|V_r| \angle 0^\circ)}{|B| \angle \theta_B}$$

$$|B| \angle \theta_B$$

$$I_R = \frac{|V_s|}{|B|} \angle \delta - \theta_B - \frac{|A||V_R|}{|B|} \angle \theta_A - \theta_B$$

$$S_{R(3\phi)} = P_{R(3\phi)} + j Q_{R(3\phi)} = 3 V_{R,ph-n} I^*$$

$$S_{R(3\phi)} = \frac{3 |V_{R,ph-n}| |V_{s,ph-n}|}{|B|} \angle \theta_B - \delta - \frac{3 |V_{R,ph-n}| |A||V_R|}{|B|} \angle \theta_B - \theta_A$$

$$V_{ph-n} = \frac{V_L}{\sqrt{3}}$$

$$S_{R(3\phi)} = \frac{|V_{R(L-L)}| |V_{s(L-L)}|}{|B|} \angle \theta_B - \delta - \frac{|A||V_{R(L-L)}|^2}{|B|} \angle \theta_B - \theta_A$$

using (1)

$$P_{R(3\phi)} = \frac{|V_{R(L-L)}| |V_{s(L-L)}|}{|B|} \cos(\theta_B - \delta) - \frac{|A||V_{R(L-L)}|^2}{|B|} \cos(\theta_B - \theta_A)$$

$$Q_{R(3\phi)} = \frac{|V_{R(L-L)}| |V_{s(L-L)}|}{|B|} \sin(\theta_B - \delta) - \frac{|A||V_{R(L-L)}|^2}{|B|} \sin(\theta_B - \theta_A)$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$V_R = DV_s - BI_s$$

$$I_R = -CV_s + AI_s$$

$$[A=D]$$

$$V_R = DV_s - BI_s \Rightarrow I_s = \frac{AV_s - V_R}{B}$$

Lossless line

$$B = jZ_0 \sin(\beta L)$$

$$A = \cos(\beta L)$$

Complex (B) j i.e.
only

$$\theta_B = 90^\circ - \text{imaginary}$$

Real (A) \cos
only

$$\theta_A = 0^\circ - \text{real}$$

$$\cos(\theta_B - \theta_A) = \cos(90) = 0$$

$$\cos(\theta_B - \delta) = \sin(\delta)$$

power Transmission Capability :-

- 1) Thermal limit
- 2) Voltage limit
- 3) stability limit

$$S_{\text{Thermal}} = \text{Thermal loading limit} = 3 V_{\text{Rated}} I_{\text{Thermal}}$$

$$P.U = \frac{\text{Actual}}{\text{Base}} \quad \text{power. unit}$$

$$V_{R(p.u)} = \frac{V_R}{V_{\text{rated}}}$$

$$V_{S(p.u)} = \frac{V_S}{V_{\text{base}}}$$

$$R_{3\phi} = \left(\frac{|V_{R(p.u)}|}{|V_{\text{rated}}|} \right) \left(\frac{|V_{S(p.u)}|}{|V_{\text{rated}}|} \right) \left(\frac{V_{\text{rated}}^2 \sin \delta}{Z_c \sin(\beta l)} \right)$$

$$= |V_{R(p.u)}| * |V_{S(p.u)}| * SIL \quad \#$$

$$P_{3\phi} = \frac{|V_S|_{p.u} * |V_R|_{p.u} * SIL \sin \delta}{\sin \left(\frac{2\pi l}{\lambda} \right)}$$


lecture
(16)

Ex (Prob. 5.8 Sadat)

3 ϕ , 765 kV, 60 Hz transposed line 4 ACSR

1,413,000 cmil, 45/7 RoboLink Cond per phase

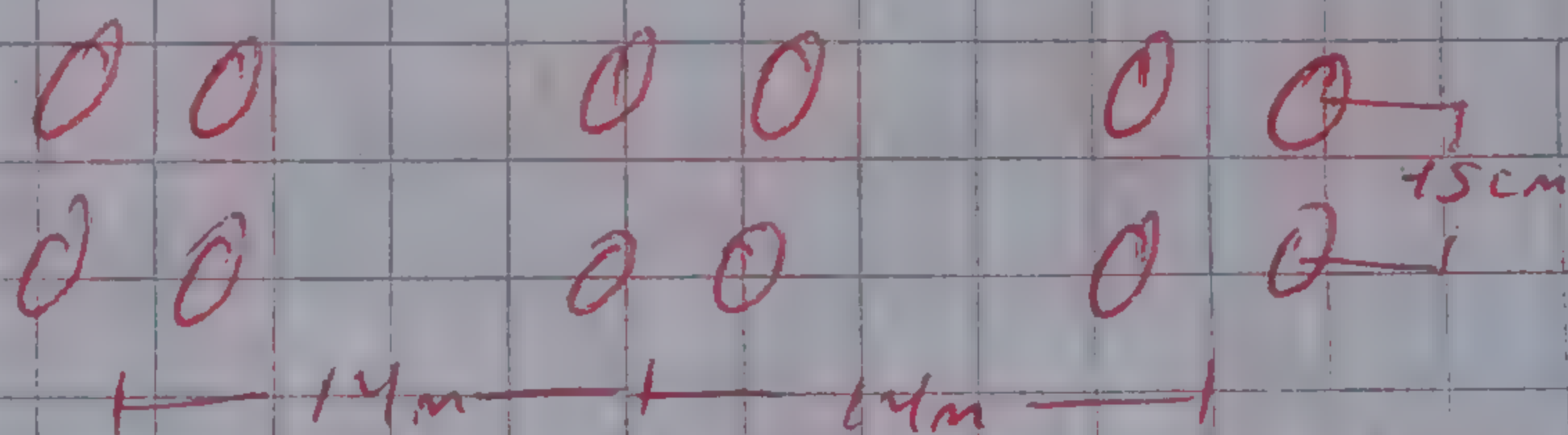spacing (14m) diameter cond (3.625 cm) and



GMR = 1.439 cm (400 km) long (lossless line)

a)

$$Z_c = \sqrt{\frac{L}{C}}$$

$$GMD = \sqrt[3]{(14)(14)(28)} = 17.63 \text{ m}$$

$$GMR = 1.09 \sqrt[4]{45^3 \times 1.439} = 0.2075 \text{ m}$$

$$L = 0.2 \ln \left(\frac{GMD}{GMR} \right) = 0.2 \ln \left(\frac{17.63}{0.2075} \right) = 0.8885 \text{ mH/km}$$

Lecture
(16)

$$GMR = 1.09 \sqrt{\frac{45^3 \times 3.625}{2}} = 0.2198 \text{ m}$$

$$C = \frac{0.0556}{\ln\left(\frac{60 \text{ m}}{GMR}\right)} = 0.01268 \mu\text{f/km}$$

ACSR

Phase

$$Z_c = \sqrt{\frac{0.8885 \times 10^{-3}}{0.01268 \times 10^{-6}}} = 264.7 \Omega$$

$$\beta = \omega \sqrt{LC} = 2\pi \times 60 \sqrt{0.8885 \times 10^{-3} \times 0.01268 \times 10^{-6}} = 0.001265 \text{ rad/km}$$

$$\beta l = \frac{0.001265 \times 180}{\pi} \times 400 = 29^\circ$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.001265} = 4967 \text{ km}$$

$$P_{TL} = \frac{765^2}{Z_c} = \frac{V_L^2}{Z_c} = 2210.89 \text{ MW}$$

$$D = \cos(\beta l) = \cos(29^\circ) = 0.8746$$

$$B = j Z_c \sin(\beta l) = j (264.7) \sin(29^\circ) = j 128.33 \Omega$$

$$C = j \frac{1}{Z_c} \sin(\beta l) = j 0.00183 \text{ S}$$

35 mH/km

$$D = A = 0.8746$$

→ this equation in ph-n
term only

$$5) V_s = A V_R + B I_R$$

$$V_R = \frac{735}{\sqrt{3}} = 424.35 \angle 0^\circ \text{ kV}$$

$$I_R = \frac{2000 \times 10^3}{\sqrt{3} \times 735 \times 10^3} = 1.571 \text{ kA} \angle -36.87^\circ$$

$$F_p = 0.8 \text{ lagging} \\ \cos^{-1}(0.8) = 36.87^\circ$$

$$|V_{s(L.L)}| = \sqrt{3} (518.86) = 896.96 \text{ kV}$$

$$V_s = (0.8746) 424.35 + j 128.33 + 1.571 \angle -36.87^\circ \\ = 518.86 \angle 18.15^\circ \text{ kV}$$

$$I_s = C V_R + D I_R$$

$$= j 0.00183 \times 424.35 \angle 0^\circ + 0.8746 \times 1.57 \angle -36.87^\circ$$

$$= 1.1 \angle -2.46^\circ$$

$$18.15 - (-2.46) = 20.6^\circ$$

$$1/P_s = \cos(20.6) =$$

$$S_{3\phi \text{ sending}} = \sqrt{3} \times 896.96 \angle 18.15^\circ + 1.1 \angle -2.46^\circ$$

any value of voltage given is line to line

$$S_{\text{out}} = 3 V_s I_s^*$$

$$= 3 \times 518.86 \angle 18.15^\circ \times 1.1 \angle 2.46^\circ$$

$$= 1709.3 \angle 20.6^\circ \text{ MVA}$$

$$= 1600 \text{ MW} + j 601.59 \text{ MVAR}$$

$$V_R = \frac{V_R(\text{NL}) - V_R(\text{FL})}{V_R(\text{FL})}$$

$$= \frac{\frac{896.96}{0.8746} - 735}{735} = 39.53\%$$

$$c) \begin{pmatrix} V_R \\ I_R \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_s \\ I_s \end{pmatrix}$$

$$AD - BC = 1$$

$$\begin{pmatrix} V_R \\ I_R \end{pmatrix} = \begin{bmatrix} 0 & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$V_R = DV_s - BI_s$$

$$V_s = \frac{765}{\sqrt{3}} = 441.67 \text{ kV} \angle 0^\circ$$

$$S_s = \sqrt{1920^2 + 1600^2} = 2011.57 \text{ MVA } \angle 17.35^\circ$$

$$S_{1\phi} = V \cdot I^*$$

$$= \frac{S^*}{\sqrt{3}} = \frac{(2011.57/3) \times 10^6 \angle -17.35^\circ}{441.67 \angle 0^\circ}$$

$$1.518 \text{ kA } \angle -17.35^\circ$$

$$V_R = DV_s - BI_s = 377.2 \angle -29.5^\circ \text{ kV}$$

$$|V_{R_{LL}}| = \sqrt{3} (377.2) = 653.329 \text{ kV}$$

$$I_R = -CV_s + AI_s = 1.749 \text{ kA } \angle -43.55^\circ$$

$$S_{R(3\phi)} = 3 V_R I_R^* = 1978.86214 \text{ MVA}$$

$$= 1920 \text{ MW} + j 479.2 \text{ MVAR}$$

Solution of last example (cont)

lecture
(17)

d) V_s, I_s, P_s, S_s with $R_L = 264.5 \Omega$ and $V_R = 735 \text{ mV}$

$$V_s = A V_R + B I_R$$

$$V_s = \frac{735}{\sqrt{3}} = 424.35 \angle 0^\circ \text{ mV (ph-n)}$$

$$I_R = \frac{V_R}{R} = \frac{735 \times 10^{-3}}{264.5} = 1604.3478 \angle 0^\circ$$

$$V_s = A V_R + B I_R = 424.42 \angle 29.02^\circ \text{ mV}$$

$$|V_{s,LL}| = \sqrt{3} \times 424.42 = 735.12 \text{ mV}$$

$$I_s = C V_R + D I_R = 1604.04 \angle 28.98^\circ \text{ A}$$

$$\cos(\phi) = \cos(29.02 - 28.98) = 0.999 \approx \pm 1 \text{ unity power factor}$$

$$S_s = 3 V_s I_s^*$$

$$= 3 (424.42 \angle 29.02^\circ) (1604.04 \angle -28.98^\circ)$$

$$= 2042.4 \angle 0.04^\circ \text{ MVA}$$

$$= 2042.4 \text{ MW} + j 1.4 \text{ MVAR}$$

$$V.R = \frac{735.12}{0.8746} - 735 \times 100 = 14.36\%$$

A

prob 5-18

power system studies on an existing system have indicated that 2400 MW are to be transmitted for distance of 400 km, the voltage level being considered include 345 kV, 500 kV and 765 kV for a preliminary design based on the practical line, loadability you may assume the following surge impedance

345 kV	$Z_c = 320 \Omega$	765 kV	$Z_c = 265 \Omega$
500 kV	$Z_c = 290 \Omega$		

$$V.R = \frac{735.12}{0.8746} - 735 \times 100 = 14.36\%$$

prob 5-18

power system studies on an existing system have indicated that 2400 MW are to be transmitted for distance of 400 km, the voltage level being considered include 345 kV, 500 kV and 765 kV for a preliminary design based on the practical line, loadability you may assume the following surge impedance

345 kV	$Z_c = 320 \Omega$	765 kV	$Z_c = 265 \Omega$
500 kV	$Z_c = 290 \Omega$		

The line wave length may be assumed to be 5000 km, the practical line loadability may be based on a load angle of 35° assume

$|V_s| = 1.0$ p.u. and $|V_r| = 0.9$ p.u. Determine

the number of 3-phase transmission circuits

required for each voltage level, each P.

transmission tower may have up to 2 cct's

To limit the corona loss, all 500 kV

line must have at least 2 conductors/phase

and all 765 kV lines must have at least

4 conductors/phase, The bundle spacing

is 45 cm, the cord size should be such

that the line would be capable of carrying current corresponding to at least 5000 MVA

چند کای = دواتر اقل

از پاور
تبدیل
در
این
قسمت

سکری لایه SIL

$$P_{3\phi} = |V_s|_{p.u.} + |V_2|_{p.u.} + SIL \sin \delta$$

$$\sin \left(\frac{2\pi}{\lambda} \right)$$

315 MW

$$SIL = \frac{K \sqrt{L_{12}}^2}{Z_c}$$

$$= \frac{345 \text{ kV}}{320} = 371.95 \text{ MVA}$$

$$P_{3\phi} = \frac{1 + 0.9 + 371.95 \sin(135)}{\sin \left(\frac{2\pi 400}{5000} \times \frac{180}{\pi} \right)}$$

$$28.8^\circ$$

$$\approx 400 \text{ MW}$$

$$\# \text{ of cct's} = \frac{2400}{4} = 6 \text{ circuits}$$

$$\# \text{ of towers} = \frac{6}{2} = 3 \text{ towers}$$

$$V_s = +3\% = 1.03 \text{ pu}$$

$$V_r = -4\% = 0.96 \text{ pu}$$

$$S_{TL} = \frac{500^2}{290} = 862.07 \text{ MVA}$$

$$P_{sf} = \frac{1 + 0.9 + 862.07 \sin(35)}{\sin(28.8)}$$

$$= 923.3 \text{ MW}$$

$$\# \text{ of circuits} = \frac{2400}{923.3} = 2.6 \Rightarrow 3 \text{ circuits}$$

$$\# \text{ of towers} = \frac{3}{2} = 1.5 \Rightarrow 2 \text{ towers}$$

$$S_{TL} = \frac{765^2}{265} = 2208.4 \text{ MVA}$$

$$P_{sf} = \frac{1 + 0.9 + 2208.4 \sin(35)}{\sin(28.8)} = 2365.2 \text{ MW}$$

$$\# \text{ of circuits} = 1 \text{ ct}$$

$$\# \text{ of towers} = 1 \text{ tower}$$

So 765
is the
best one

$$I = \frac{5000}{\sqrt{3} \times 765} = 3773.5 \text{ A / phase}$$

$$I = \frac{3773.5}{4} = 943.38 \text{ A / conductor}$$

From table see which and here this value

شنت + كيفية
Capacitor
نظير T.L (مكافئ) بالتيار

كيف نظير X_L و X_C نظير

lecture
(18)

Line Compensation

Shunt reactor




V

light load (no load) so
voltage increase
(loaded line)
Low voltage so
add capacitor

Shunt capacitor



V

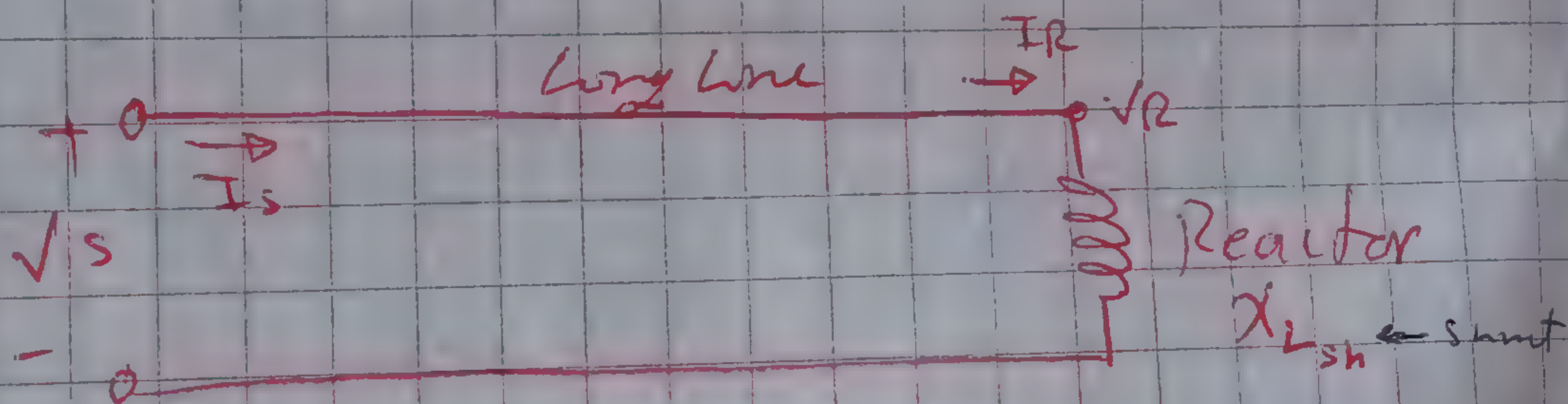

$$I_R = \frac{V_R}{jX_{L_{sh}}} \quad (1)$$

$$V_s = A V_R + B I_R$$

$$= \cos(\beta l) V_R + j Z_c \sin(\beta l) I_R \quad (2) \quad \text{lossless}$$

sub (1) in (2)

$$V_s = \left[\cos(\beta l) + \frac{Z_c \sin(\beta l)}{X_{L_{sh}}} \right] V_R \quad (3)$$

Assume V_R and V_S are in phase

So the power through T.L is zero

From (3)

$$X_{L_{sh}} = \frac{\sin(\beta l)}{\frac{V_S}{V_R} - \cos(\beta l)} \cdot Z_c \quad (6)$$

For $V_S = V_R$

$$X_{L_{sh}} = \frac{\sin(\beta l)}{1 - \cos(\beta l)} Z_c$$

To find the relation between I_S and I_R

$$I_S = C V_R + D I_R$$

$$= j \frac{1}{Z_c} \sin(\beta l) V_R + \cos(\beta l) I_R \quad (4)$$

Sub (1) in (4)

$$V_S = \left[-\frac{1}{Z_c} \sin(\beta l) X_{L_{sh}} + \cos(\beta l) \right] I_R \quad (5)$$

sub (6) in (5)

$$I_s = -I_R$$

at mid span
(T.L. at (2.25))
 $I = 0$

$$V_m = \frac{V_R}{\cos(\beta \frac{L}{2})}$$

mid point

in lecture 13

Example 8 For T.L of EXL) calculate

a) the receiving end voltage when line is terminated in an open circuit and is overvoltage with 500 kV at the sending end

b) Determine the reactance and MVAR of 300 Shunt reactor to be installed at the receiving end to keep the no load receiving end voltage at the rated value

$$Z_L = 290.43 \Omega$$

$$\beta L = 21.64$$

$$V_s = 500 \text{ kV}$$

open ckt $\Rightarrow I_R = 0$ (no load)

the receiving end voltage

$$V_{R(NL)} = \frac{V_s_{\text{ph-n}}}{A} = \frac{288.675 \times 10^3}{0.9295} = 310.57 \text{ kV (ph-n)}$$

$$V_s = \frac{500}{\sqrt{3}} = 288.675 \text{ kV}$$

$$A = \cos(\beta L) = 0.9295$$

$$|V_{R(NL)}|_{L-L} = \sqrt{3} (310.57) = 537.9 \text{ kV}$$

$$X_{L_{sn}} = \frac{\sin(21.64)}{1 - \cos(21.64)} \times 290.43$$

$$= 1519.5 \Omega$$

$$Q = \frac{V_{LL}^2}{X} = \frac{500^2}{1519.5} = 164.53 \text{ MVAR}$$

For 3 ϕ

no load, zero load, capacitor, reactor, series, shunt

lecture
(19)

shunt capacitor compensation

$$P_{R(3\phi)} = \frac{|V_{S(L)}||V_{R(L)}| \cos(\theta - \delta)}{|B|} - \frac{|A||V_{R(L)}|^2 \cos(\theta - \delta)}{|B|}$$

$$\rightarrow P_{R(3\phi)} = \frac{|V_{S(L)}||V_{R(L)}| \sin \delta}{X} \quad \text{lossless line}$$

$$Q_{R(3\phi)} = \frac{|V_{S(L)}||V_{R(L)}| \sin(\theta - \delta)}{|B|} - \frac{|A||V_{R(L)}|^2 \sin(\theta - \delta)}{|B|}$$

$$\rightarrow Q_{R(3\phi)} = \frac{|V_{S(L)}||V_{R(L)}| \cos \delta}{|B|} - \frac{|V_{R(L)}|^2 \cos(\beta)}{X} \quad \text{lossless line}$$

(X = B)

Series capacitor compensation :-

- 1) Are connected in series with the line
 - 2) Are located at the mid point of the line
- used for :-

are used to reduce the series reactance

Percentage Compensation = $\frac{X_{cser}}{X}$

between the load and supply point

- 2) Improve steady state and transient stability
- 3) More economical loading
- 4) Minimum voltage dip on load buses

Example 8 A transmission line in ex. 5.5) Lecture (13)

supplies a load of 1000 MVA, 0.8 p.f lagging at 500 kV, a) Determine the MVAR and the capacitance of the shunt capacitor to be installed at the receiving end voltage at 500 kV when the line is energized with 500 kV at the sending end

b) only series capacitor are installed at the mid point of the line providing 40% compensation, find the sending end voltage and V.R

Lagging = inductive load
 Leading = capacitive load

$$Z_c = 290.43 \Omega, \quad \beta_1 = 21.64^\circ$$

$$\cos^{-1}(0.8) = 36.87^\circ$$

$$S_r = 1000 \angle 36.87^\circ = 800 \text{ MW} + j 600 \text{ MVAR}$$

$$\begin{aligned} a) \quad B = X &= Z_c \sin(\beta_1) = 290.43 * \sin(21.64^\circ) \\ &= 107.11 \Omega \end{aligned}$$

$$P_{r(3\phi)} = \frac{|V_{S(L-L)}| |V_{R(L-L)}|}{X} \sin \delta$$

$$800 \text{ MW} = \frac{(500 \text{ kV})(500 \text{ kV})}{107.11} \sin \delta$$


$$\delta = 20.04^\circ$$

$$Q_{r(3\phi)} = \frac{|V_{S(L-L)}| |V_{R(L-L)}|}{|B|} \cos(\delta) - \frac{|V_{R(L-L)}|^2}{X} \cos(\beta_1)$$


$$= \frac{(500 \text{ kV})(500 \text{ kV}) \cos(20.04^\circ)}{107.11} - \frac{500^2 \cos(21.64^\circ)}{107.11}$$

$$= 23.187 \text{ MVAR}$$

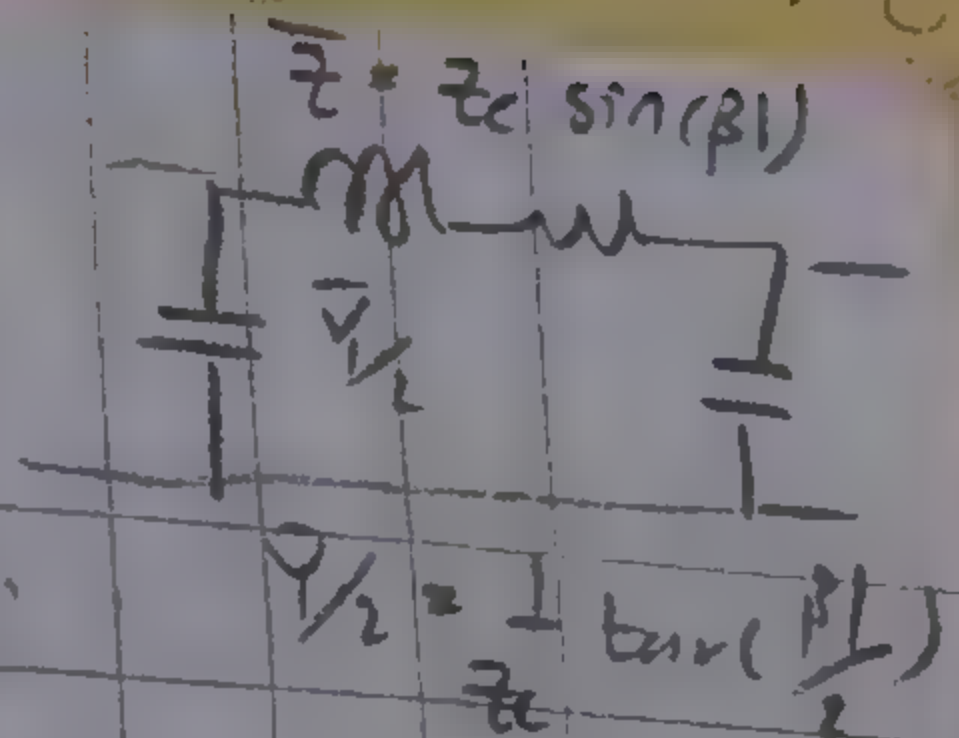$+V_e = C \sin(\text{leading})$ P_f $C \sin$



at the receiving end

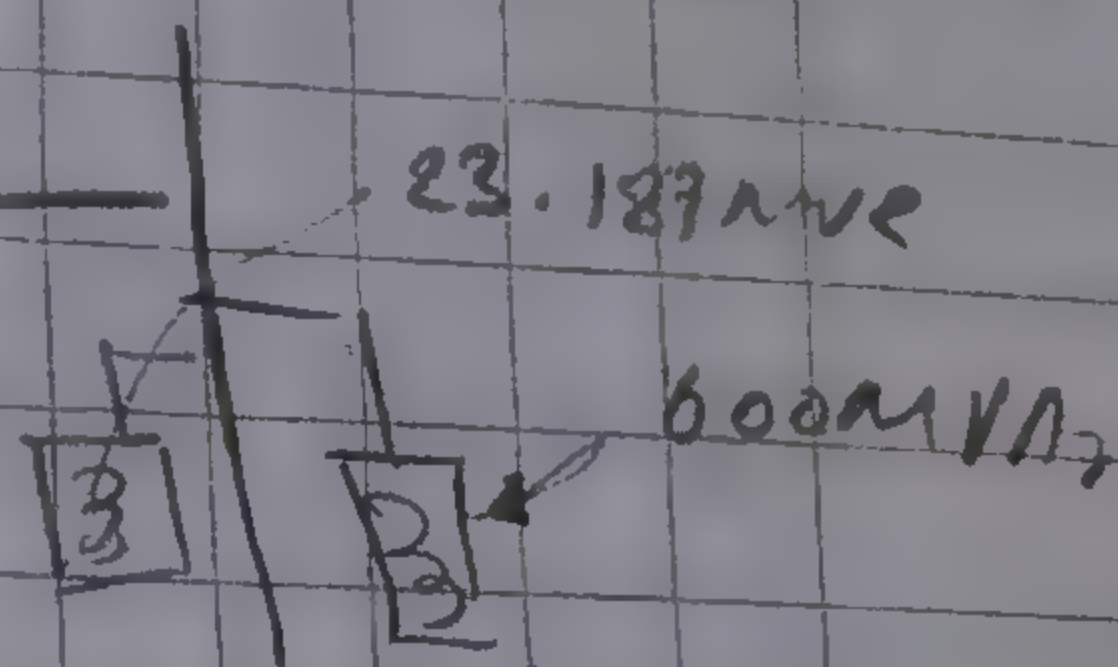

The required capacitor MVAR

$$P_f (\text{cap}) = -j23.187 \times -j600 = -j576.85 \text{ MVAR}$$

$$X_c = \frac{V_R^2}{Q} = \frac{500^2}{576.85} = 433.38 \Omega$$

$$C = \frac{1}{\omega X_c} = \frac{1}{2\pi \times 60 \times 433.38} = 6.1 \mu\text{f}$$

$$40\% = \frac{X_{c \text{ ser}}}{X} = \frac{X_{c \text{ ser}}}{107.11} \Rightarrow X_{c \text{ ser}} = 42.84 \Omega$$

compensator, \bar{V}_e (receiving end)

$$V_s = A V_R + B I_R$$

$$A = 1 + \frac{\bar{Z} \bar{Y}}{2}, \quad B = \bar{Z}, \quad C = \bar{Y} (1 + \frac{\bar{Z} \bar{Y}}{2})$$

$$D = A$$

$$S = 3 V_R I^*$$

$$\bar{Z} = \bar{Z} = j107.11 - j42.84 = j64.27 \Omega$$

$$\bar{Y} = \frac{2}{Z_c} \tan\left(\frac{\beta l}{2}\right) = \frac{2}{290.43} \tan\left(\frac{21.04^\circ}{2}\right)$$

$$\bar{Y} = 0.001316 \text{ S}$$

$$A = 1 + \frac{\bar{Z}\bar{Y}}{2} = 0.9577$$

$$B = \bar{Z} = j64.27 \Omega$$

$$V_R = \frac{500 \text{ W}}{\sqrt{3}} = 288.675 \text{ W} \angle 0^\circ$$

$$I_R = \frac{1000 \angle -36.87^\circ}{3 \times 288.675 \angle 0^\circ} = 1.155 \angle -36.87^\circ \text{ A}$$

$$V_S = 326.4 \angle 10.47^\circ \text{ W}$$

$$|V_{S(LL)}| = \sqrt{3} (326.4) = 565.4 \text{ W}$$


$$\%V_R = \frac{V_R(NL) - V_R(FL)}{V_R(FL)} \times 100$$

$$V_R(NL) = \frac{V_S}{A} = \frac{565.4}{0.9577} = 590.37 \text{ W}$$

$$\%VR = \frac{590.37 - 500}{500} \times 100 = 18\%$$

Prob 5-15 Saadat

Lecture (20)

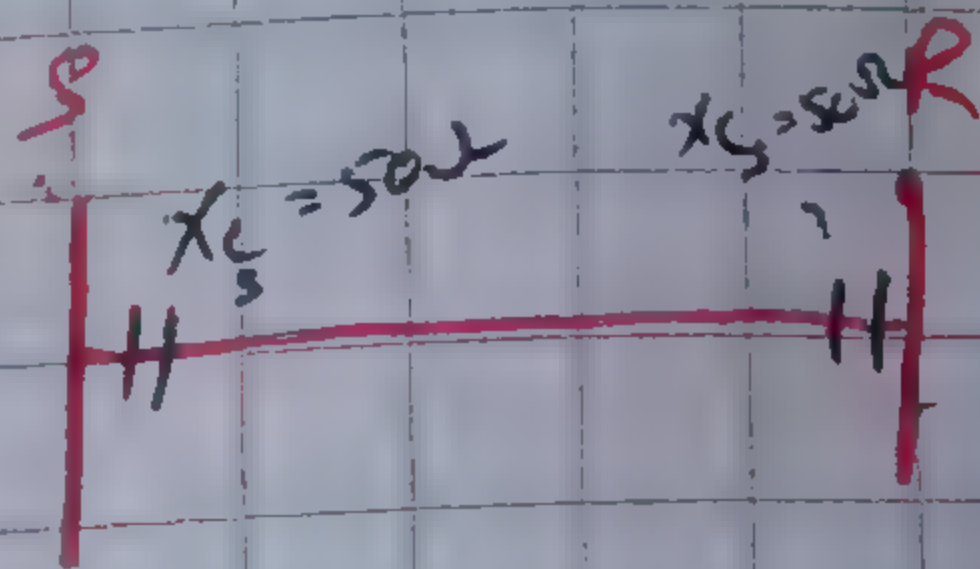

$$A = D = 0.86 + j0.0$$

$$B = 0 + j130.2 \Omega$$

$$C = j0.002 \text{ S}$$

a) V_s , I_s , P_s , S_s and V_R

b) by adding series capacitor at the two ends

Find $ABCD$ constant

$$\begin{bmatrix} \bar{A} & \bar{B} \\ \bar{C} & \bar{D} \end{bmatrix} = \begin{bmatrix} 1 & -j50 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0.86 & j130.2 \\ j0.002 & 0.86 \end{bmatrix} \begin{bmatrix} 1 & -j50 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 0.96 & j39.2 \\ j0.002 & 0.96 \end{bmatrix}$$


$$V_{s_{\text{new}}} = \bar{A} V_s + \bar{B} I_R$$

Prob 5-12 Saadat

$$B = X = 128.33 \Omega$$

$$\beta = 29$$

$$Z_c = 264.7 \Omega$$

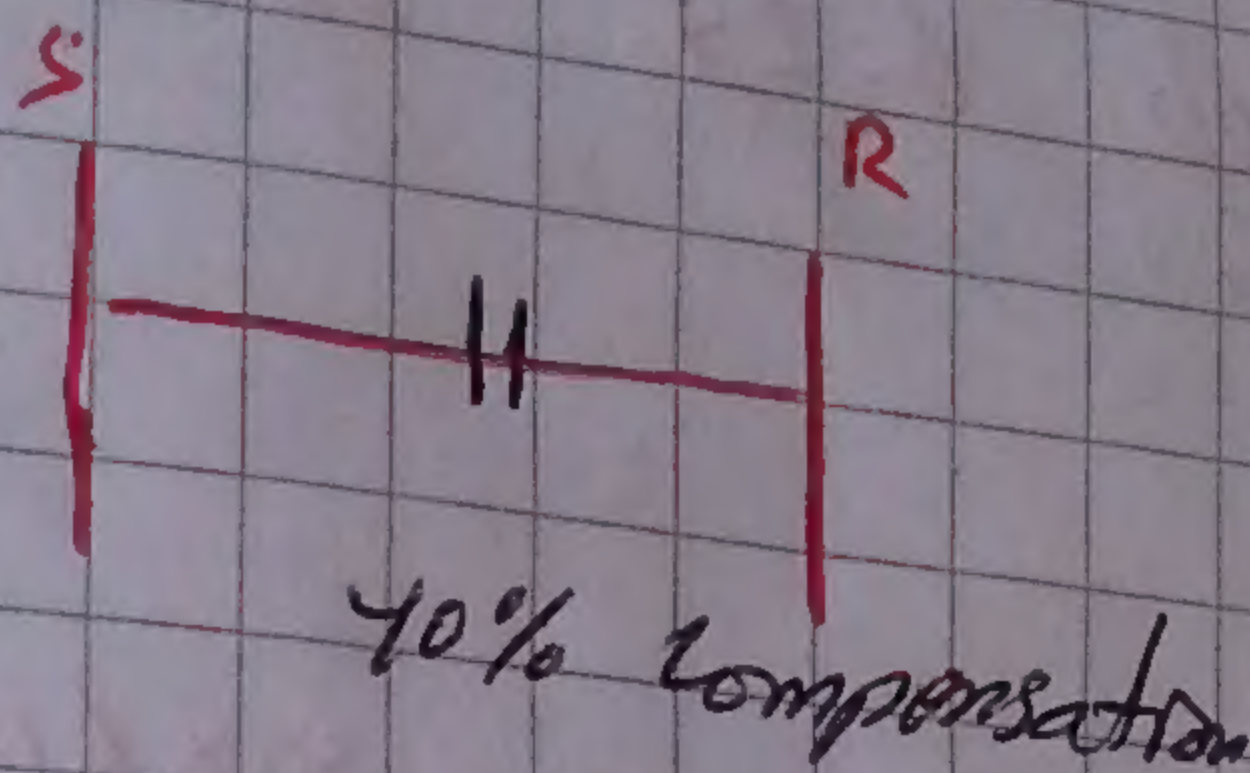

$$40\% = \frac{X_{c \text{ series}}}{X}$$

$$X_{cs} = 0.4 \times 128.33 = 51.33 \Omega$$

$$C = \frac{1}{\omega X_c} = 51.67 \mu F$$

$$\bar{Z} = j(128.33 - 51.33) = j77 \Omega$$


$$\bar{Y} = \frac{2}{jZ_c} \tan\left(\frac{\beta l}{2}\right) = \frac{2}{j264.7} \tan\left(\frac{29}{2}\right) = j0.001954$$

$$A = 1 + \frac{(j77)(j0.00195)}{2} = 0.92476$$

$$B = \bar{Z} = j77 \Omega$$

$$C = \bar{Y} \left(1 + \frac{\bar{Z}^2}{4}\right) = 0.00188$$

prob 6-25 star

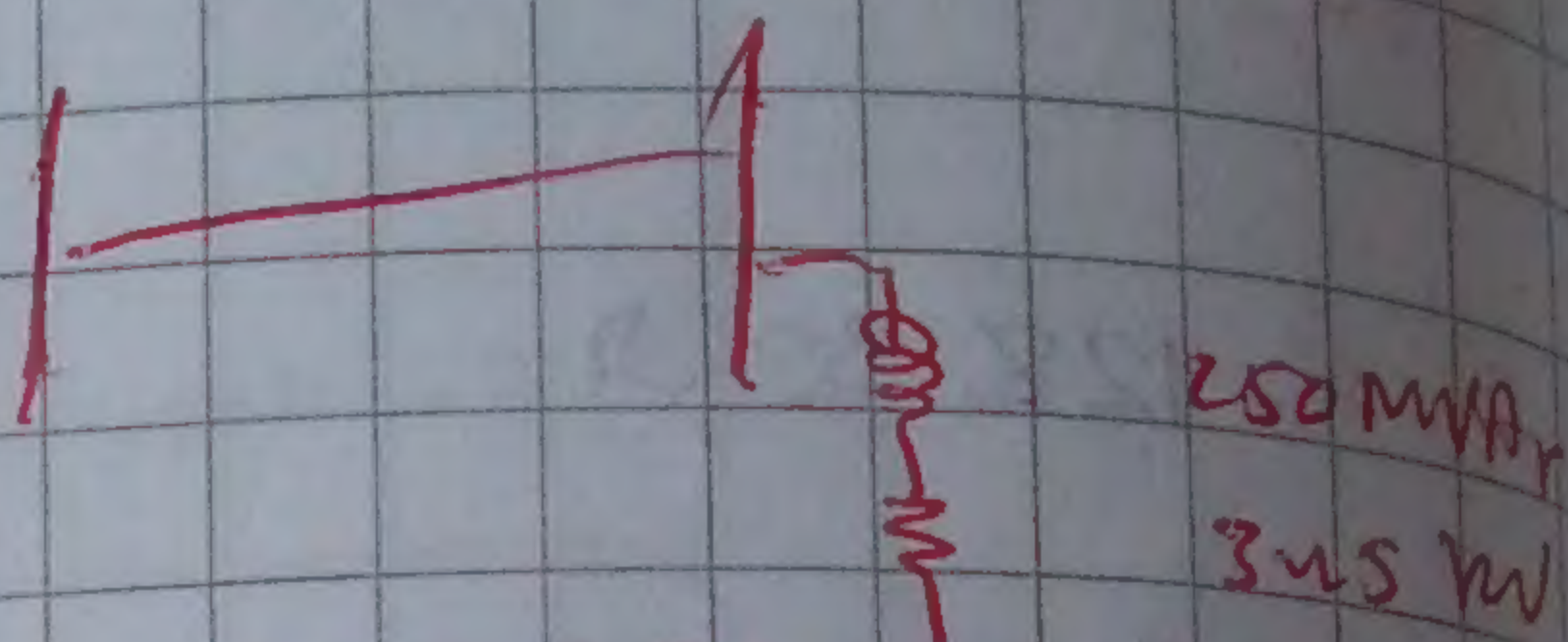

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.818 \angle 1.3 & 172.2 \angle 84.2 \\ 0.001933 \angle 90.4 & 0.818 \angle 1.3 \end{bmatrix}$$

$$X_L = \frac{345}{250} = 476.1 \angle 90$$


$$B_L = \frac{1}{X_L} = \frac{1}{476.1 \angle 90} = 0.0021 \angle -90 = -j0.0021$$

$$\begin{bmatrix} \hat{A} & \hat{B} \\ \hat{C} & \hat{D} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j0.0021 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1.178 \angle -0.88 & 172.2 \angle 84.2 \\ 0.000217 \angle 83.25 & 1.178 \angle -0.88 \end{bmatrix}$$

prob

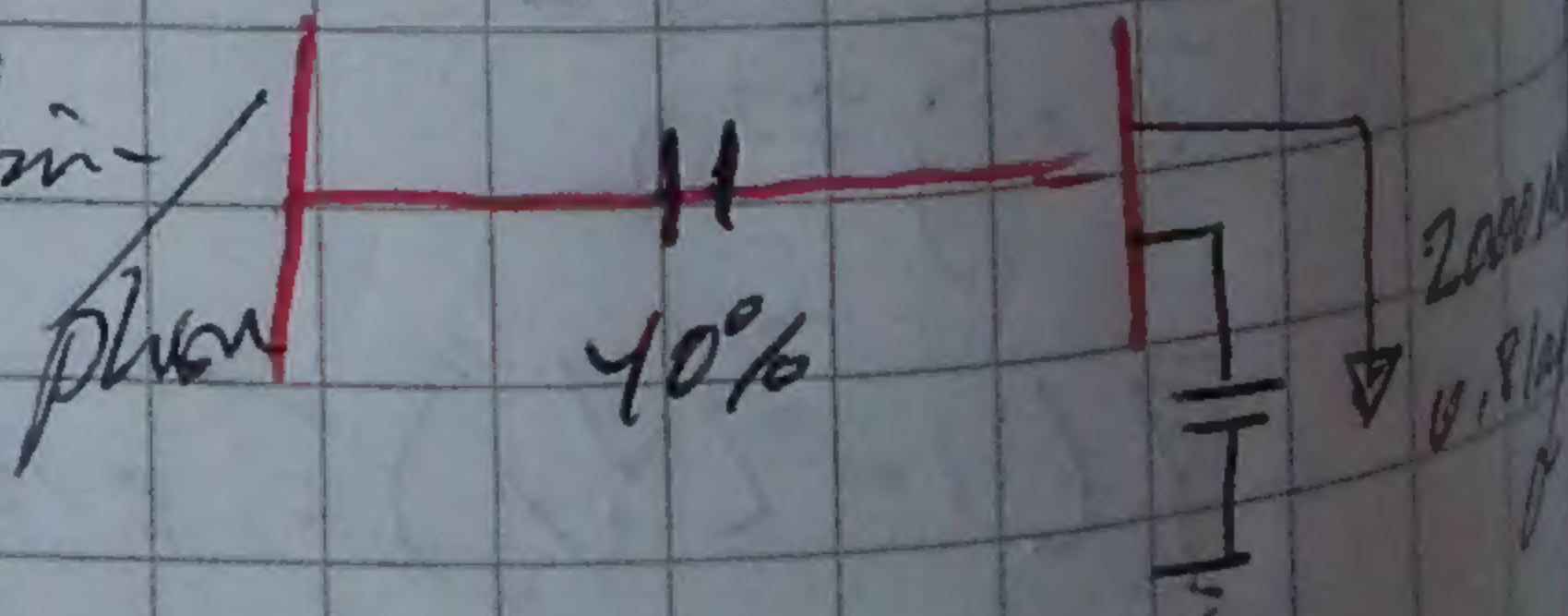Find total MW and capacitor
of series and shunt capacitor
to keep $V_R = 735$ kV where
 $V_S = 785$ kV where $X = 128.33 \Omega$



$$P_{\frac{P}{3\phi}} = \frac{|V_s| |V_R|}{X} \sin \delta$$

$$Q_{\frac{P}{3\phi}} = \frac{|V_s| |V_R|}{1.81} \cos \delta - \frac{|V_R|^2}{X} \cos(\beta_1)$$

Line-line

$$2000 \angle 36.86^\circ = 1600 + j1200$$

$$\begin{aligned} X_{\text{new}} &= 128.33 \\ &= 0.1(128.33) \\ &= j7.72 \end{aligned}$$


$$1600 = \frac{(765)(735)}{j7.72} \sin \delta$$

$$\delta = 12.656^\circ$$

$$Q_{\frac{P}{3\phi}} = \frac{(765)(735) \cos(12.656) - \frac{(735)^2}{7.72} \cos(29)}{}$$

$$= 636.75 \text{ MVAR}$$
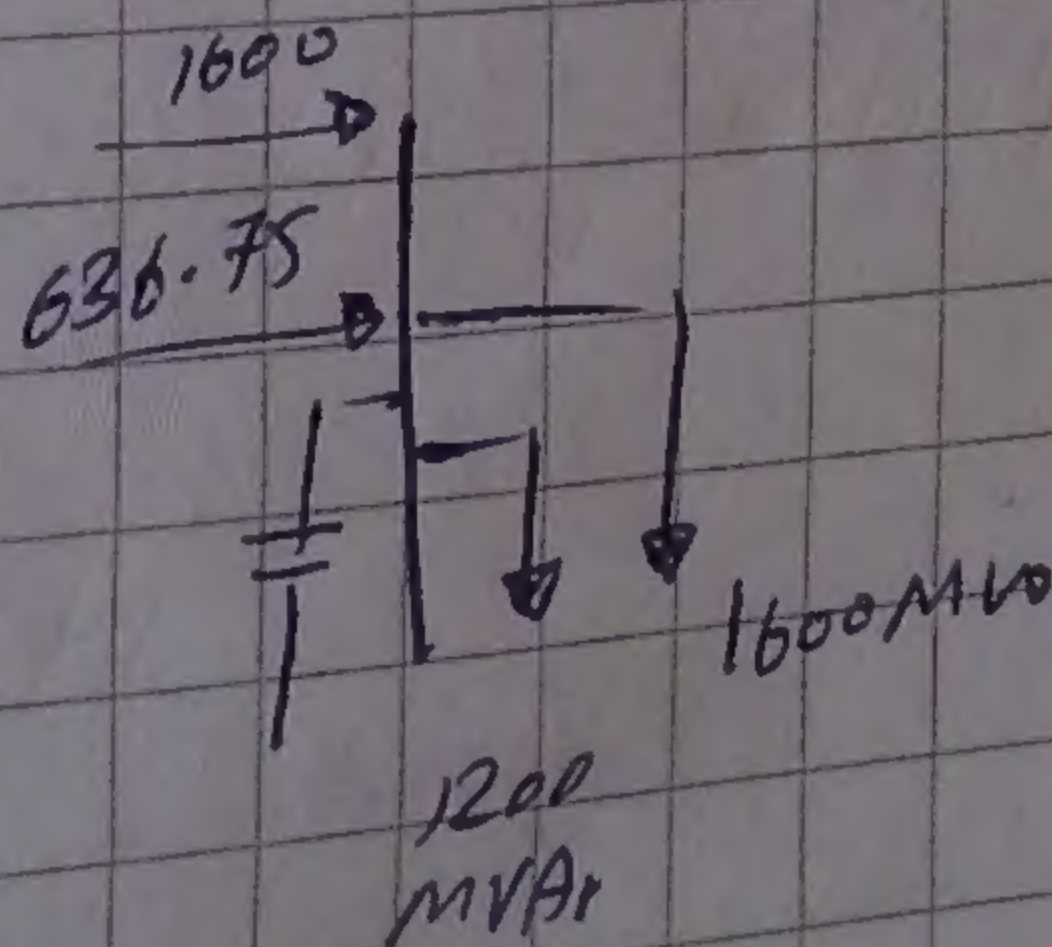
$$j636.75 - j1200 = -j563.25 \text{ MVAR}$$



$$X_L = \frac{735^2}{563.25} = -j959.12 \Omega$$

2000 MVA
0.8 lag
 α

$$S_R = 1600 + j 636.75$$

$$I_{R_{new}} = \frac{S_R^*}{3 \sqrt{2}}$$

$$I_{R_{new}} \quad (A)$$

see problem 6.6 step (8)